

## Principles of Electrical Engineering I – TOOLS

**Fundamental Laws:** Kirchoff's current and voltage laws

Using the above fundamental laws, we have the following techniques or tools that we can utilize to do circuit analysis:

- Voltage and current divider rules,
- Series and parallel combination of resistances,
- $\Delta$ -Y transformations,
- Node voltage method,
- Mesh current method,
- Source transformations,
- Thevenin and Norton equivalents,
- Superposition theorem.

Some of the above tools are direct analysis methods, and some others are tools to simplify network analysis. The name of the game in circuit or network simplification is constructing **network equivalents** which when appropriately done can simplify the analysis, while providing more insight into the network behavior.


Not only, we need to be very familiar with all the above tools, but also we need to know when to use what tool. Analogous to a mechanic using correctly a particular tool for a particular task, we need to learn to pick correctly an appropriate tool that suits a particular circuit. This comes only by experience. To get such an experience, one needs to do a lot of home-work problems.

Once you learn driving an automobile, you can drive on any road. Once you understand and learn fundamental methods of circuit analysis, you can solve any circuit. Two most commonly used fundamental methods of circuit analysis are **Node voltage method** and **Mesh current method**. You need to understand the intricacies of these two methods very well.

# Principles of Electrical Engineering I
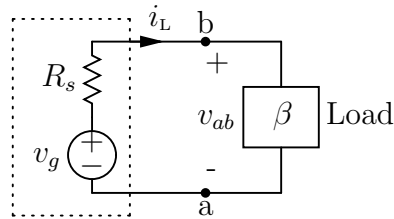
## Source Transformations

Voltage Source in series with a resistance



Defining equation between  $v_{ab}$  and  $i_L$ :

$$v_{ab} = v_g - i_L R_s$$

Graphical representation of the defining equation:


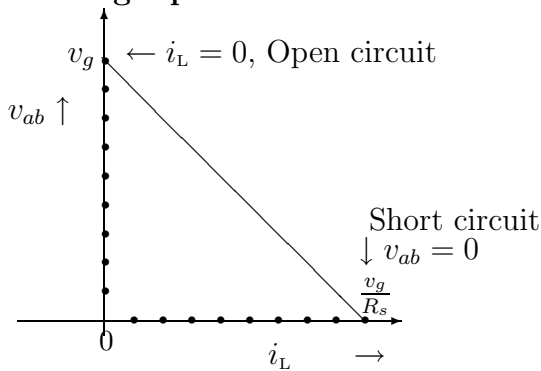


Figure 1

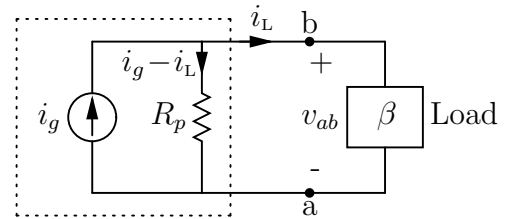Current Source in parallel with a resistance



Defining equation between  $v_{ab}$  and  $i_L$ :

$$v_{ab} = i_g R_p - i_L R_p$$

Graphical representation of the defining equation:

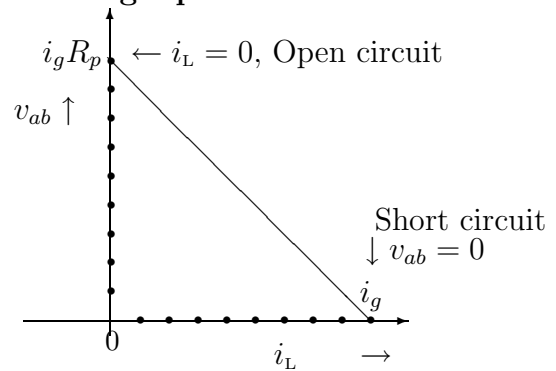


Figure 2

**When can the two circuits be equivalent with respect to the terminals a and b?**

**They are equivalent if  $v_{ab}$  versus  $i_L$  characteristics of both are identical.**

$$v_g = i_g R_p \quad \text{and} \quad \frac{v_g}{R_s} = i_g.$$

$$\frac{i_g R_p}{R_s} = i_g \Rightarrow R_p = R_s.$$

$$\frac{v_g}{R_s} = i_g \Rightarrow v_g = i_g R_p$$

## Source Transformations – Example

**Example.** Determine the current  $i_o$  shown in Figure (a) given below.

A series of transformations are given below.

Think of how equivalents are determined

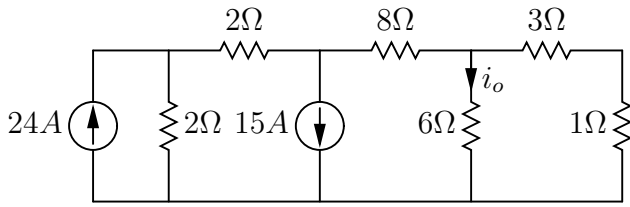


Fig. (a)

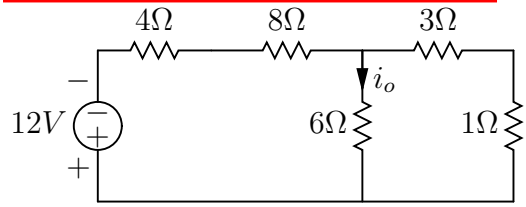


Fig. (d)

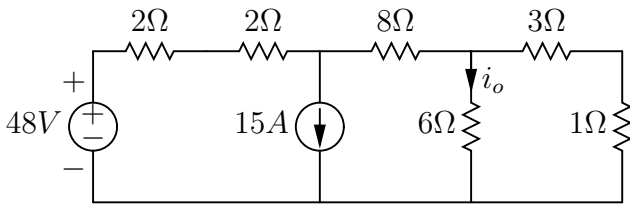


Fig. (b)

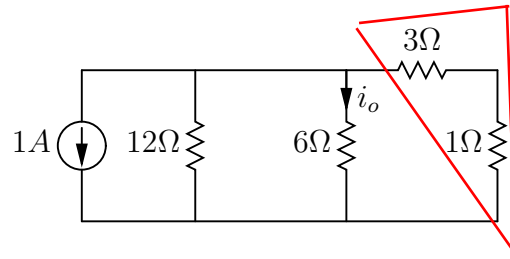


Fig. (e)

Combine into one resistance

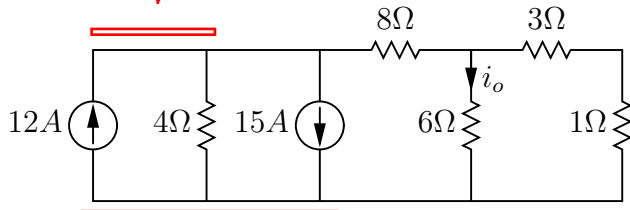


Fig. (c)

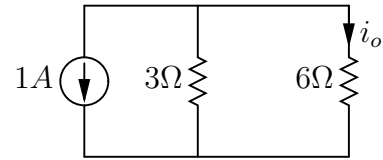


Fig. (f)

Combine the current sources into one source, and then use source transformation to get Figure (d)

**Example:** Our interest in this problem is to determine the currents  $i_x$  and  $i_y$  in the circuit shown in Figure 1. For this purpose we simplify the circuit as much as we can, solve the simple circuit and then come back to solve the given circuit.

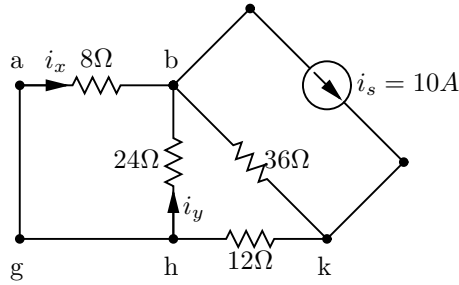


Figure 1



Source transformation

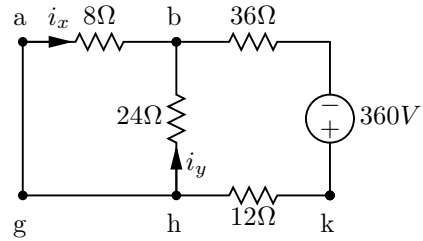


Figure 2



Source Transformation

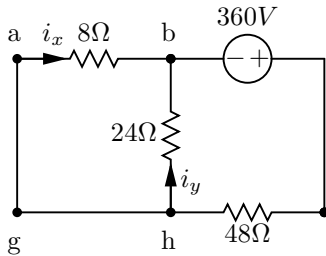


Figure 3

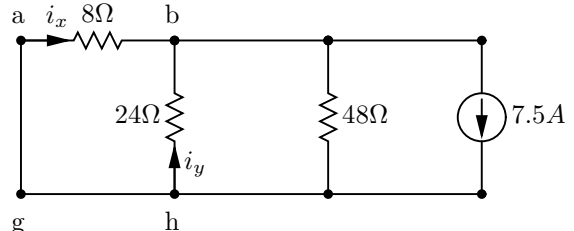


Figure 4

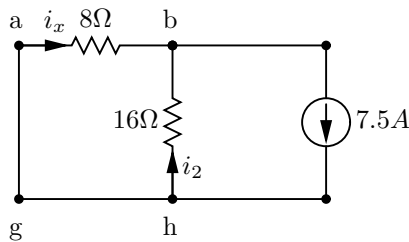


Figure 5

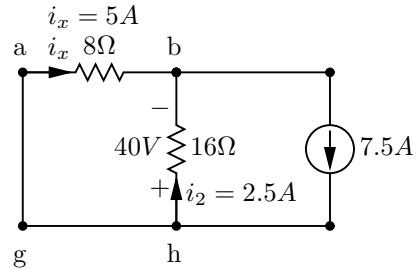


Figure 6

In the above analysis, we successively simplified the given circuit into simpler circuits. Finally, we solved a simple circuit as in Figure 6. To determine other currents in the circuit of Figure 1, we need to trace back from the simple circuit of Figure 6 to the circuit of Figure 5, and so on.

Let us consider the circuit of Figure 4 as re-drawn below on the left side. We can evaluate the current from node h to node b via  $24\Omega$  in two ways. Knowing the voltage across  $24\Omega$  as  $40\text{ V}$ , we note the current from node h to node b as  $\frac{5}{3}\text{ A}$  by simple Ohm's law. Or we can evaluate it by current division rule by knowing the current  $2.5\text{ A}$  splits into two parts, one part going through  $24\Omega$  and the other part going through  $48\Omega$ . This enables us to determine all currents in the circuit of Figure 1 as shown below on the right side.

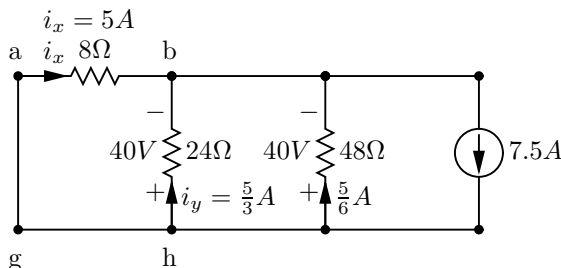


Figure 4 re-drawn

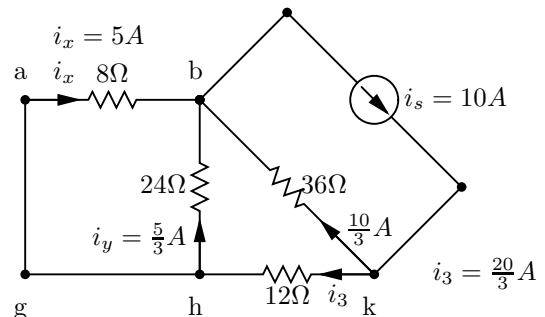



Figure 1 re-drawn

## Principles of Electrical Engineering I

### A Caution About Circuit Equivalentents

**Caution:** The circuit  $\alpha$  in Figure is a fixed circuit and the circuit  $\beta$  is a load on the circuit  $\alpha$ . Suppose we intend to determine an equivalent of the fixed circuit  $\alpha$  with respect to the terminals a and b. This can be done only when the circuit  $\alpha$  does not have **any controlling variables** that control some dependent source which is in the circuit  $\beta$ . The reason is simple. If you attempt to do so, you will immediately realize that the access to the controlling variable is lost and you will not know how to characterize the dependent source which is in the circuit  $\beta$ .

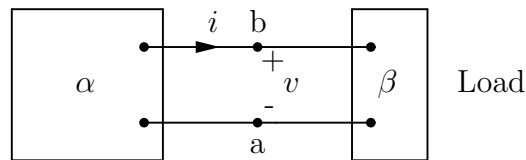**This caution applies to Thevenin and Norton equivalentents as well as Source Transformations.**




Figure

# Principles of Electrical Engineering I

## Thevenin Theorem

Consider the interconnection of two circuits  $\alpha$  and  $\beta$  as shown in Figure 1. The circuit  $\alpha$  is a given circuit while the circuit  $\beta$  is a load on the circuit  $\alpha$ . We would like to analyze the interconnected circuit to determine  $v$  and  $i$  at the terminals a and b where the two individual circuits are interconnected. We would like to do so for different types of loads (i.e. as the circuit  $\beta$  changes). This implies that we need to repeat the circuit analysis to determine  $v$  and  $i$  every time the circuit  $\beta$  changes.

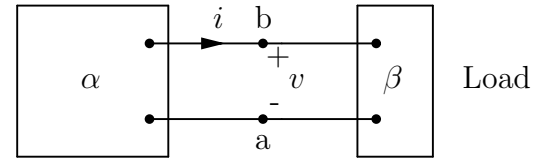


**Figure 1**

To reduce the computational burden of repetitive circuit analysis, Thevenin came up with a remarkable and highly useful result which gives a simple equivalent circuit for the circuit  $\alpha$ . Before stating Thevenin's results, let us impose a mild condition on the circuit  $\alpha$ .

**Assumption:** Let  $\alpha$  be a linear circuit which could be passive or active. If it is active, let both the controlling and controlled branches be contained within it. Let there be no restrictions on the circuit  $\beta$ .

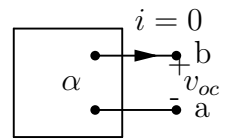
**Open circuit voltage  $v_{oc}$ :**

The voltage across the terminals a and b when the load  $\beta$  is an open circuit and thus draws no current can obviously be called as the open circuit voltage, and it is often denoted by  $v_{oc}$ .



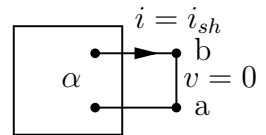
**Short circuit current  $i_{sh}$ :**

The current from b to a when the load  $\beta$  is a short circuit and thus has no voltage across it can obviously be called as the short circuit current, and it is often denoted by  $i_{sh}$  or  $i_{sc}$  as in the text book.



**Thevenin's Theorem:** The circuit  $\alpha$ , however complex it might be, is equivalent to a voltage source (denoted by  $v_{Th}$ ) in series with a resistance (denoted by  $R_{Th}$ ) between the terminals a and b as depicted in Figure 2. The voltage source  $v_{Th}$  equals the open circuit voltage  $v_{oc}$ . The resistance  $R_{Th}$  equals the ratio of open circuit voltage  $v_{oc}$  to the short circuit current  $i_{sh}$ . It is also the resistance of the circuit  $\alpha$  seen at the terminals a and b when all the **independent** voltage as well as current sources in the circuit  $\alpha$  are set to zero.

**Equivalent of Circuit  $\alpha$**

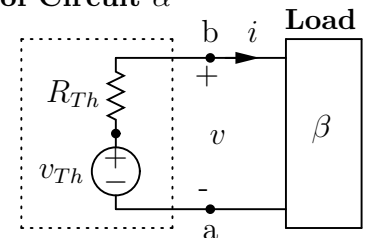


**Figure 2**

**Proof of Thevenin's Theorem:**

If we accept the fact that the circuit  $\alpha$ , however complex it might be, can be represented by the simple circuit of Figure 2, we can then easily prove  $v_{Th} = v_{oc}$  and  $R_{Th} = \frac{v_{oc}}{i_{sh}}$ .

Obviously, if the circuit  $\beta$  is an open circuit, the voltage  $v$  across the terminals a and b is  $v_{oc}$  and  $v_{Th}$  respectively in Figures 1 and 2. Then for the equivalence of the circuits in Figures 1 and 2, we must have  $v_{Th} = v_{oc}$ . Let us next assume that the circuit  $\beta$  is a short circuit. Then the current  $i$  is  $i_{sh}$  in Figure 1, and it is  $\frac{v_{oc}}{R_{Th}}$  in Figure 2. This implies that for the equivalence of the circuits in Figures 1 and 2, we must have  $R_{Th} = \frac{v_{oc}}{i_{sh}}$ .

## Thévenin-Norton Equivalency

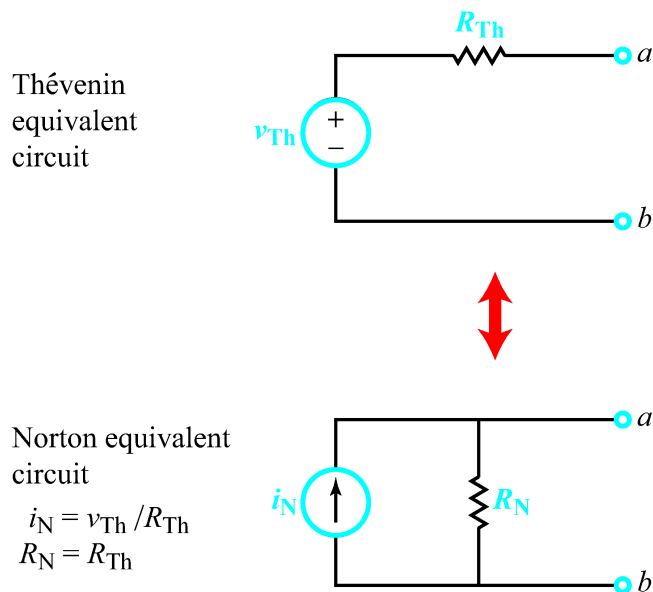


Equivalence between Thévenin and Norton equivalent circuits.

### 332:221 Principles of Electrical Engineering I

The formulae related to  $\Delta$ -Y equivalents are given below:

$$\begin{array}{l|l}
 R_1 = \frac{R_b R_c}{R_a + R_b + R_c} & R_a = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_1} \\
 R_2 = \frac{R_a R_c}{R_a + R_b + R_c} & R_b = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_2} \\
 R_3 = \frac{R_a R_b}{R_a + R_b + R_c} & R_c = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_3}
 \end{array}$$

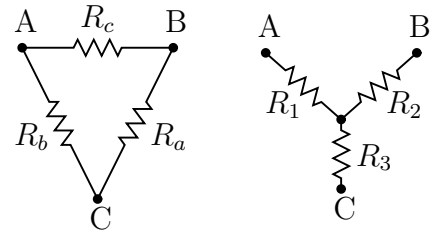

**Problem:** Our interest in this problem is to determine the Thevenin Equivalent circuit at the terminals A and B of the circuit shown in Figure 1. You can solve for open circuit voltage  $v_{oc}$  and short circuit current  $i_{sh}$  by different methods, including Node voltage method and mesh current method. The answers are  $v_{oc} = 6.66$  V and  $i_{sh} = 2.4$  A (see next page for the details of Node voltage method). In what follows, we will determine Thevenin resistance  $R_{Th}$  at the terminals A and B by constructing an independent source-less circuit as shown in Figure 2. For clarity, the circuit of Figure 2 is re-drawn as in Figure 3. In order to determine the resistance between the terminals A and B, we need a  $\Delta$  to Y transformation. We can transform the  $\Delta$  between the terminals A, C, and G (comprising of resistances  $9\Omega$ ,  $1\Omega$ , and  $6.25\Omega$ ), to a Y as shown in Figure 4. Here  $R_1$ ,  $R_2$ , and  $R_3$  are respectively given by

$$R_1 = \frac{9}{16.25}\Omega, \quad R_2 = \frac{9(6.25)}{16.25}\Omega, \quad R_3 = \frac{6.25}{16.25}\Omega.$$

Finally, from Figure 4, we can determine the resistance between the terminals A and B by series-parallel combinations as

$$R_{Th} = 2.775\Omega.$$

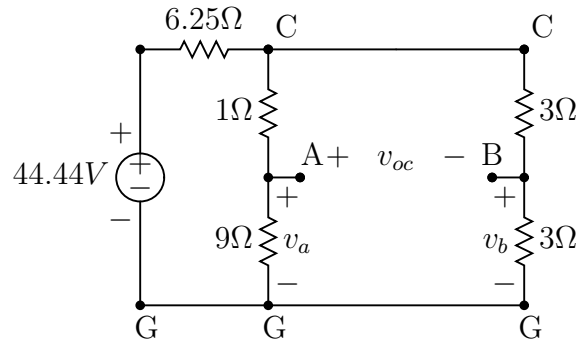


Figure 1

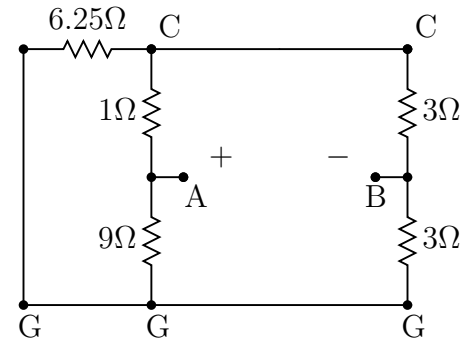


Figure 2

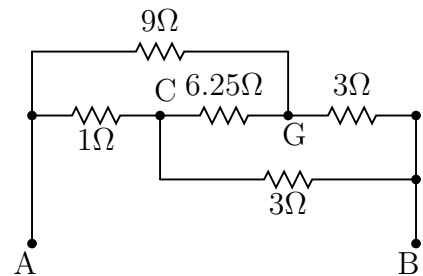


Figure 3

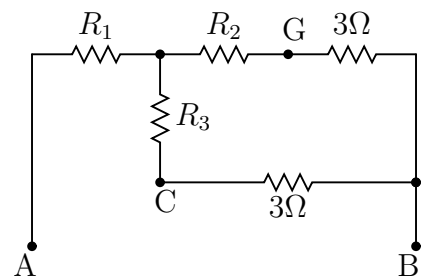


Figure 4



**Determination of Open Circuit Voltage  $v_{oc}$  by Node voltage method:** Consider the circuit of Figure 5 where node voltages  $v_s$ ,  $v_a$ ,  $v_b$ , and  $v_c$  are marked while taking node G as the reference node. We note that  $v_s = 44.44$  V. We can easily write the following three node equations:

$$\begin{aligned} \frac{v_a}{9} + \frac{v_a - v_c}{1} &= 0 \\ \frac{v_b}{3} + \frac{v_b - v_c}{3} &= 0 \\ \frac{v_c - 44.44}{6.25} + \frac{v_c - v_a}{1} + \frac{v_c - v_b}{3} &= 0. \end{aligned}$$

By solving the above equations, we get  $v_{oc} = v_a - v_b = 6.66$  V. In fact, we have  $v_a = 15$  V,  $v_b = 8.33$  V, and  $v_c = 16.66$  V.

**Determination of Short Circuit Current  $i_{sh}$  by Node voltage method:** Consider the circuit of Figure 6 where node voltages  $v_s$ ,  $v_a$ ,  $v_b$ , and  $v_c$  are marked while taking node G as the reference node. We note that  $v_s = 44.44$  V and  $v_a = v_b$ . We can easily write the following three node equations:

$$\begin{aligned} \frac{v_a}{9} + \frac{v_a - v_c}{1} + i_{sh} &= 0 \\ \frac{v_b}{3} + \frac{v_b - v_c}{3} - i_{sh} &= 0 \\ \frac{v_c - 44.44}{6.25} + \frac{v_c - v_a}{1} + \frac{v_c - v_b}{3} &= 0. \end{aligned}$$

By solving the above equations, we get  $v_a = v_b = 10.8$  V and  $v_c = 14.4$  V. This yields  $i_{sh} = 2.4$  A, and thus  $R_{Th} = \frac{v_{oc}}{i_{sh}} = \frac{6.66}{2.4} = 2.775\Omega$ .

**Home-work (not collected):** Determine Open Circuit Voltage  $v_{oc}$  and Short Circuit Current  $i_{sh}$  by Mesh Current Method.

**Solution:**

$$v_c = 16.66V, v_b = 8.33V, v_a = 15V$$

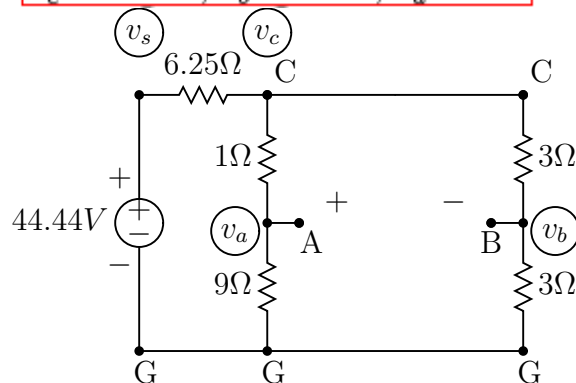


Figure 5

**Solution:**

$$v_c = 14.4V, v_a = v_b = 10.8V$$

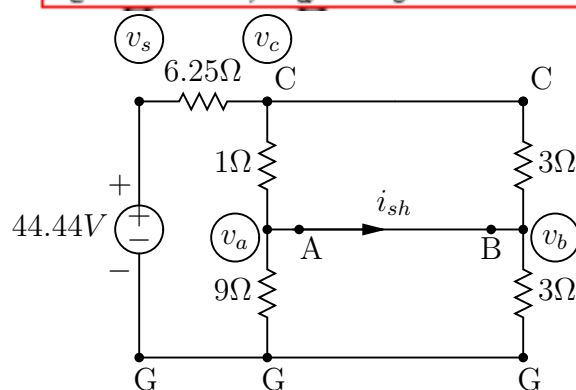


Figure 6

## Thevenin Equivalent Circuit – Example

We would like to determine the Thevenin equivalent circuit at the terminals F and H.

**Determination of  $v_{oc}$  by Mesh current method:** We select two mesh currents  $i_1$ , and  $i_2$  as shown. The dependent voltage source  $1.25i_1$  is controlled by  $i_1$  which is one of the assumed mesh currents. We note also that the independent current source  $2A$  is related to the assumed mesh currents by the equation,

$$i_1 + i_2 = -2.$$

Besides the above equation, we need one KVL equation to solve for the two unknowns  $i_1$  and  $i_2$ . The KVL can be written for the loop ABCDEGA (Super mesh of ABCGA and GCDEG),

$$3 + 1.25i_1 - i_1 \cdot 2 - 12 + i_2 \cdot 4 = 0 \Rightarrow -0.75i_1 + 4i_2 = 9.$$

By solving the above equations, we get

$$i_1 = -\frac{17}{4.75} = -3.579A, \quad i_2 = 1.579A.$$



The voltage rise from F to H  $v_{oc} = 1.25i_1 - 2i_1 = 2.6842V$ .

**Determination of  $R_{Th}$  by using a test source:**

The independent voltage sources are set to zero, i.e. a short is placed in their locations. The independent current source is set to zero, i.e. it is opened. The resulting circuit is shown on the right where a test voltage of 1 V between the terminals F and H is applied. It is easy to compute  $i_1$  as 0.25A and current in  $2\Omega$  resistance from D to C as 0.34375A. Hence  $i_{test} = 0.59375A$ . As such

$$R_{Th} = \frac{1}{0.59375} = 1.6842\Omega.$$

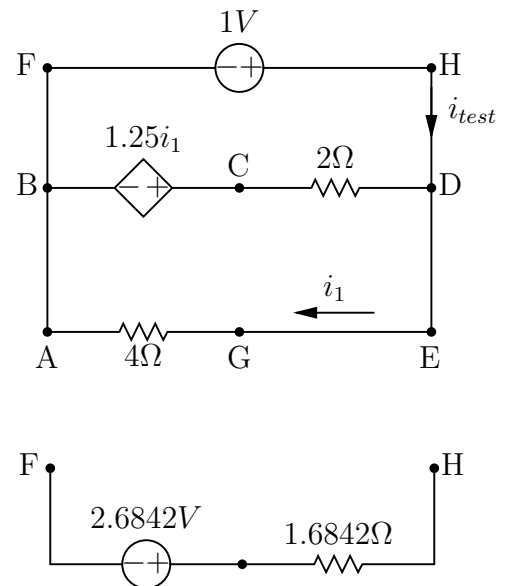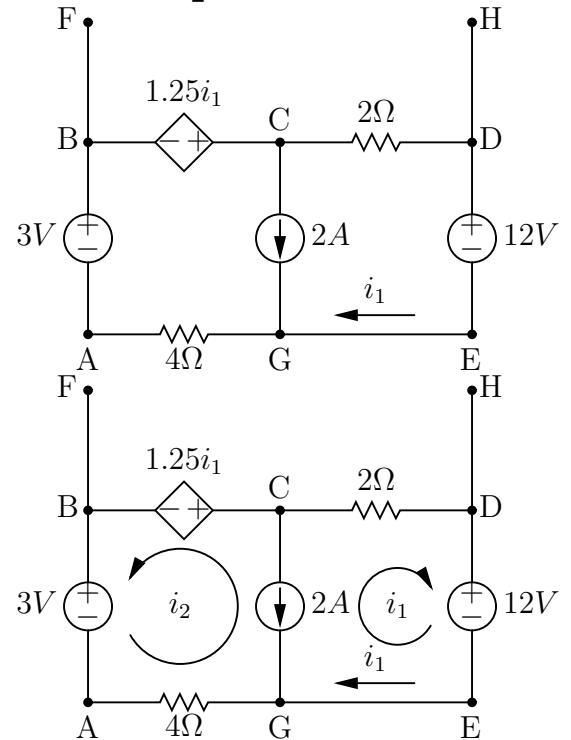The Thevenin equivalent circuit is shown on the right.



**Determination of  $i_{sh}$  by Mesh current method:** In this example, one can easily determine  $i_{sh}$  by inspection. For example, by writing the KVL for the loop ABFHDEGA, we can first determine  $i_2$ . Then by writing KCL at node G, we can determine  $i_1$ . Once  $i_1$  is known, we can determine  $i_{sh}$  by writing the KVL for the loop BCDHFB.

To use the Mesh current method systematically, we start by selecting three mesh currents  $i_1$ ,  $i_2$ , and  $i_{sh}$  as shown. The dependent voltage source  $1.25i_1$  is controlled by  $i_1$  which is one of the assumed mesh currents. We note also that the independent current source  $2A$  is related to the assumed mesh currents by the equation,

$$i_1 + i_2 = -2.$$

Besides the above equation, we need two KVL equations to solve for the three unknowns  $i_1$ ,  $i_2$ , and  $i_{sh}$ . The KVL can be written for the loop ABFHDEGA (Super mesh of ABCGA, GCDEG, and FHDCBF),


$$3 - 12 + i_2 4 = 0.$$

Also, the KVL can be written for the mesh BCDHFB,

$$1.25i_1 - (i_1 + i_{sh})2 = 0.$$

By solving the above equations, we get  $i_1 = -4.25$ ,  $i_2 = 2.25$ , and  $i_{sh} = 1.59375$  A. We can now easily verify that
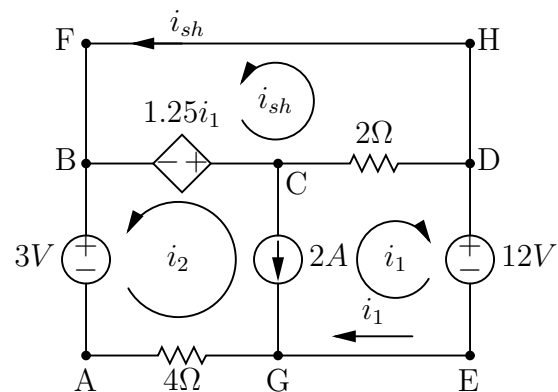
$$R_{Th} = \frac{v_{oc}}{i_{sh}} = 1.6842\Omega.$$



# Principles of Electrical Engineering I

## Example – Thevenin Equivalent Circuit

**Fall 1999 quiz:** Determine the Thevenin equivalent circuit of the circuit shown in Figure 1 with terminal b positive with respect to a.

**Node Voltage Method to determine  $v_{OC}$ :** In Figure 2, pertinent node voltage variables are marked by selecting node a as the reference node. We can easily determine  $i_x$  as

$$i_x = \frac{8 - v_{OC}}{3}$$

Also, we can write the node equation at node b as

$$\frac{v_{OC} - 3i_x}{2} + \frac{v_{OC} - 8}{3} = 0.$$

By solving the above two equations, we get

$$v_{Th} = v_{OC} = 5V.$$

**Node Voltage Method to determine  $i_{sh}$ :** In Figure 3, pertinent node voltage variables are marked by selecting node a as the reference node while shorting the nodes a and b. We can easily determine  $i_x$  as

$$i_x = \frac{8 - 0}{3}A.$$

Also, we can write the node equation at node b as

$$\frac{0 - 3i_x}{2} + \frac{0 - 8}{3} + i_{sh} = 0.$$

By solving the above two equations, we get

$$i_{sh} = \frac{20}{3}A.$$

Then, the Thevenin resistance  $R_{Th}$  is given by

$$R_{Th} = \frac{v_{OC}}{i_{sh}} = 0.75\Omega.$$

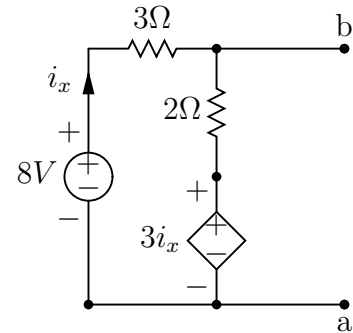


Figure 1

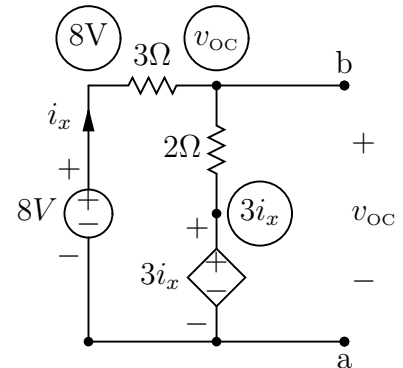


Figure 2


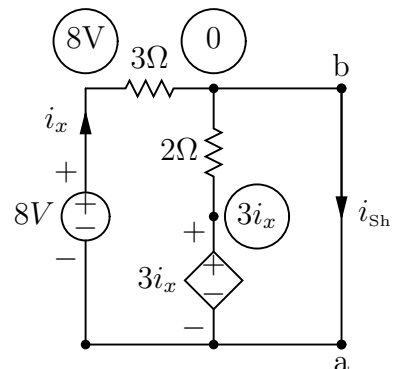


Figure 3

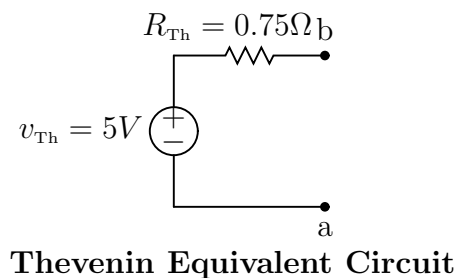

Thevenin Equivalent Circuit

**Fall 1999 quiz:** We determine next the Thevenin equivalent circuit of the circuit shown in Figure 1 while using Mesh Current method.

**Mesh Current Method to determine  $v_{OC}$ :** In Figure 4, mesh current  $i_x$  is marked (Note that there is only one mesh). We can easily write the mesh equation as

$$8 - 3i_x - 2i_x - 3i_x = 0.$$

This yields  $i_x = 1$  A. We note that

$$v_{OC} = 3i_x + 2i_x = 5V.$$

**Mesh Current Method to determine  $i_{sh}$ :** In Figure 5, Mesh Current variables are marked while shorting the nodes a and b (Note that there are now two meshes, and hence there are two mesh current variables,  $i_x$  and  $i_{sh}$ ). We can easily write the two mesh equations as

$$\begin{aligned} 8 - 3i_x - 2(i_x - i_{sh}) - 3i_x &= 0 \\ 3i_x - 2(i_{sh} - i_x) &= 0. \end{aligned}$$

By solving the above two equations, we get

$$i_x = \frac{8}{3} A \quad \text{and} \quad i_{sh} = \frac{20}{3} A.$$

Then, the Thevenin resistance  $R_{TH}$  is given by

$$R_{TH} = \frac{v_{OC}}{i_{sh}} = 0.75\Omega.$$

**Test Voltage and Test Current Method to determine  $R_{TH}$ :** Figure 6 shows the set up. We can easily write the two KCL equations as

$$\begin{aligned} v_t + 3i_x &= 0 \\ v_t - 2(i_x + i_t) - 3i_x &= 0. \end{aligned}$$

By solving the above two equations, we get

$$i_x = -\frac{v_t}{3} \quad \text{and} \quad i_t = \frac{4v_t}{3}.$$

Then, the Thevenin resistance  $R_{TH}$  is given by

$$R_{TH} = \frac{v_t}{i_t} = \frac{3}{4} = 0.75\Omega.$$

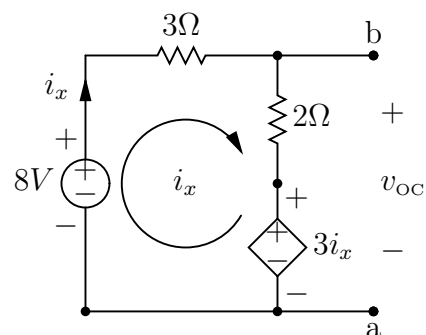


Figure 4


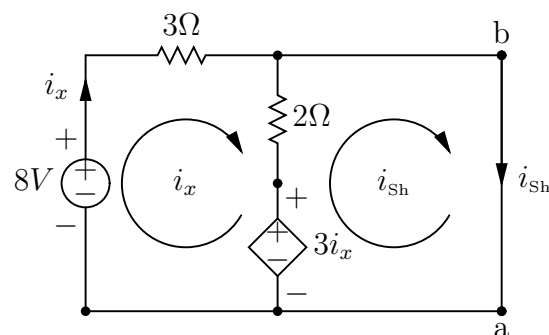


Figure 5

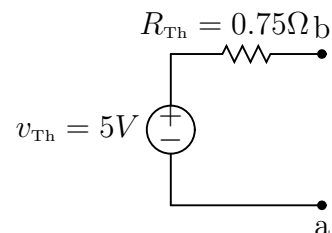

Thevenin Equivalent Circuit

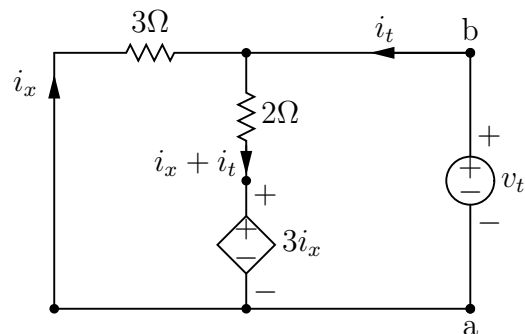


Figure 6


## Thevenin Equivalent Circuit – Example

We would like to determine the Thevenin equivalent circuit at the terminals a and b. To do so, we plan to compute all of the following three: (1) open circuit voltage, (2) short circuit current, and (3) Thevenin resistance  $R_{Th}$  directly.
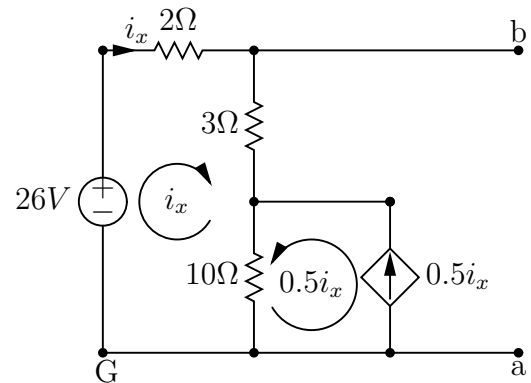
### Determination of open circuit voltage $v_{oc}$ :

Using mesh current analysis, determine the open circuit voltage  $v_{oc}$  between the terminals a and b. Choose appropriate mesh currents in any direction you like. None of the methods other than mesh current analysis are acceptable.

There are two meshes and we chose  $i_x$  and  $0.5i_x$  as mesh currents as shown.



One obvious KVL equation can be written as

$$26 = 2i_x + 3i_x + 10\left(\frac{3}{2}i_x\right).$$


This gives us  $i_x = 1.3$  A. We can then compute

$$v_{oc} = 26 - 2i_x = 23.4V$$
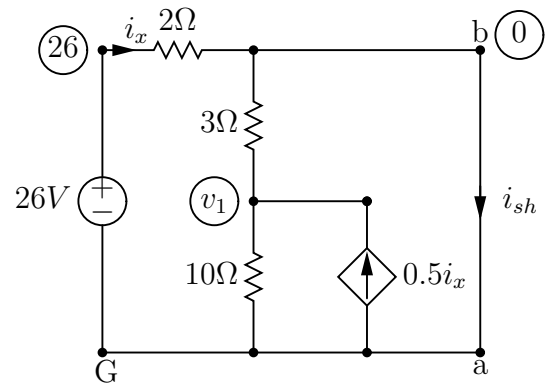
### Determination of short circuit current $i_{sh}$ :

Using nodal analysis, determine the short circuit current  $i_{sh}$  from the terminal a to b. Using G as the reference, choose appropriate node voltages you like. None of the methods other than nodal analysis are acceptable.

Using G as the reference, we can mark easily node voltages as shown. It is easy to compute



$$i_x = \frac{26}{2} = 13A.$$

Also, we can write the KCL equation at the node marked by  $v_1$  as

$$\frac{v_1}{3} + \frac{v_1}{10} - 0.5i_x = 0 \Rightarrow v_1 = 15V.$$

By writing the KCL equation at the top node of  $3\Omega$  resistance, we get

$$i_{sh} = i_x + \frac{v_1}{3} \Rightarrow i_{sh} = 18A.$$

**Direct determination of  $R_{Th}$  from the independent source-less network:** The independent source-less network can be constructed as shown on the right side. Determine  $i_{test}$  by any method. Show all your work. We can mark by inspection, the branch currents as shown. Also,

$$i_x = -\frac{1}{2}A.$$

Then, by writing one of the KVL equations, we get

$$1 = 3(i_x + i_{test}) + 10\left(\frac{3}{2}i_x + i_{test}\right) \Rightarrow i_{test} = 0.7692A$$

Determine the Thevenin resistance  $R_{Th}$  as



$$R_{Th} = \frac{1}{i_{test}} = \frac{1}{0.7692} = 1.3\Omega.$$

The value for  $R_{Th}$  as calculated from  $\frac{v_{oc}}{i_{sh}}$  is

$$R_{Th} = \frac{v_{oc}}{i_{sh}} = \frac{23.4}{18} = 1.3\Omega.$$

Yes, both ways of computing  $R_{Th}$  agree with each other.

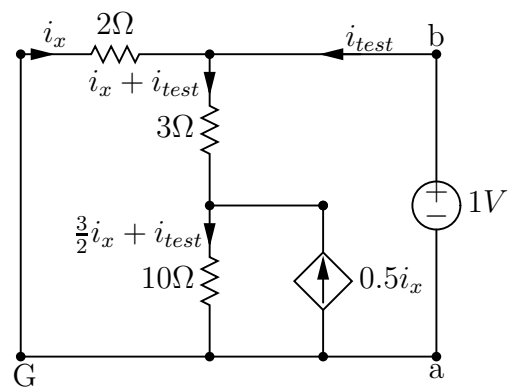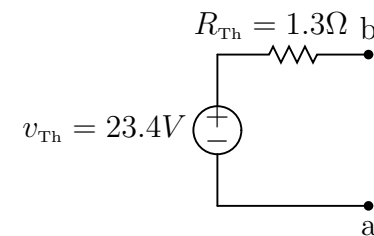Mark appropriate values for the Thevenin equivalent circuit shown on the right.



## Thevenin Equivalent Circuit – Example

We would like to determine the Thevenin equivalent circuit at the terminals a and b. To do so, we need to compute open circuit voltage and short circuit current.

**Determination of  $v_{oc}$  by Node voltage method:** Using G as the reference, we mark the node voltages as shown. Here  $v_b$  and  $v_1$  are unknown. We note that  $v_b = v_{oc}$ . We need to express the controlling current  $i_1$  in terms of the node voltages. We see easily that  $i_1 = v_b - 2$ . Also, we note that  $v_1 = v_b - 2i_1 = v_b - 2(v_b - 2) = 4 - v_b$ . We can now easily write the node equation at the nodes K, L, and M (all of them as one node) as

$$\frac{v_b - 16}{2} + \frac{v_1}{2} + \frac{v_b - 2}{1} = 0.$$

We can substitute for  $v_1$  as  $4 - v_b$ , and rewrite the above equation as

$$\frac{v_b - 16}{2} + \frac{4 - v_b}{2} + \frac{v_b - 2}{1} = 0.$$

By solving which we get  $v_b = v_{oc} = 8V$ .

**Determination of  $v_{oc}$  by Mesh current method:** We select two mesh currents  $i_1$  and  $i_2$  as shown. The dependent voltage source  $2i_1$  is controlled by  $i_1$  which is one of the assumed mesh currents. To solve for the two currents  $i_1$  and  $i_2$ , we need to write two KVL equations. The KVL for the loop LKGPL can be written as



$$-i_1 - 2 - 2(i_1 + i_2) + 2i_1 = 0 \Rightarrow i_1 + 2i_2 = -2.$$

Similarly, the KVL for the loop MNPLM can be written as

$$-2i_2 - 16 - 2(i_1 + i_2) + 2i_1 = 0 \Rightarrow 4i_2 = -16.$$

From the second equation, we get  $i_2 = -4A$ . Substituting this in the first equation, we get  $i_1 = 6A$ . Knowing  $i_2 = -4A$ , we get


$$v_{oc} = 16 + 2i_2 = 8V.$$

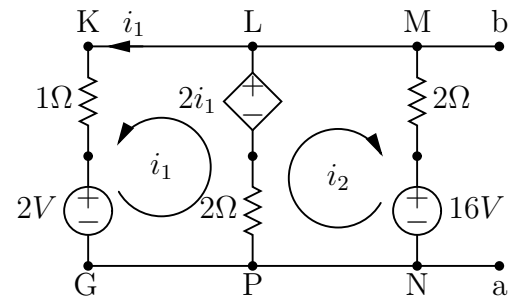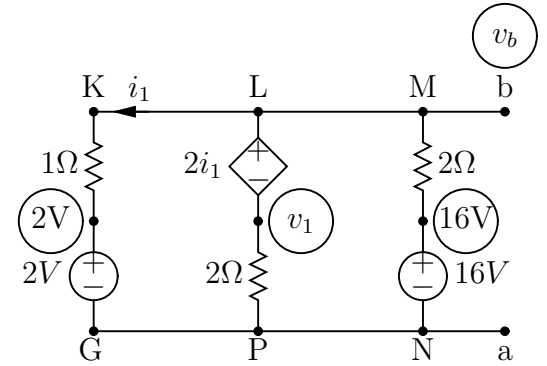



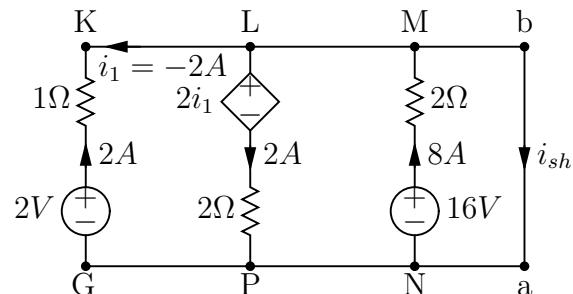**Determination of short circuit current  $i_{sh}$ :**

The short circuit current  $i_{sh}$  can be easily calculated by inspection. (You can try other methods to compute  $i_{sh}$ .) To do so, at first, we calculate the current in each branch. By writing the loop equation GKLMbaNPG, we see the current from G to K as 2 A. Similarly, by writing the loop equation LMbaNPL, we see the current from L to P as 2 A. Finally, by writing the loop equation MbaNM, we see the current from N to M as 8 A. We observe  $i_{sh} = 8 + 2 - 2 = 8$  A.



The Thevenin resistance  $R_{Th}$  is given by



$$R_{Th} = \frac{v_{oc}}{i_{sh}} = \frac{8}{8} = 1\Omega.$$

**Determination of  $R_{Th}$  by using a test source:**

The independent voltage sources are set to zero, i.e. a short is placed in their locations. The resulting circuit is shown on the right where a test voltage of 1 V between the terminals F and H is applied. It is easy to compute  $i_1$  as 1A. Knowing  $i_1$ , we see easily that the current from P to L as  $\frac{1}{2}$  A. Also, we see the current from M to N as  $\frac{1}{2}$  A. Then, writing the KCL equation at the nodes K, L, and M (all of them as one node), we see  $i_{test} = 1$  A. This implies that

$$R_{Th} = \frac{1}{1} = 1\Omega.$$

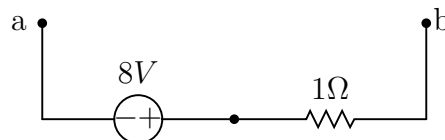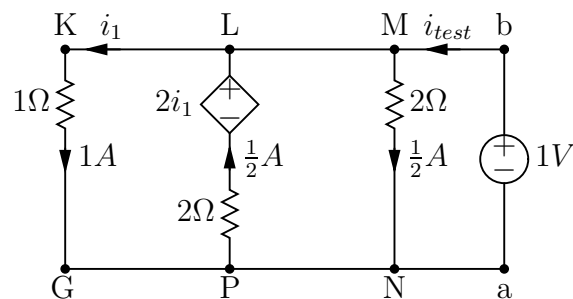The Thevenin equivalent circuit is shown on the right.



# Principles of Electrical Engineering I

**Example 1:** The purpose of this example is to show that  $v_{OC}$  is zero whenever there are no independent sources in the given circuit, and to illustrate that  $R_{Th}$  could be negative whenever active elements are present.

Determine the open circuit voltage  $v_{OC}$  at the terminals a and b for the circuit of Figure 1a.

**Determination of  $v_{OC}$ :** To determine  $v_{OC}$ , take g as the reference node and mark the node voltages as shown in Figure 1b. Obviously,

$$i_x = \frac{v_{OC}}{10}, \quad \text{and} \quad v_1 = v_{OC} - 16i_x = -0.6v_{OC}.$$

Thus,

$$i_1 = \frac{v_1}{1} = -0.6v_{OC}$$

Now the node equation at b or a implies that

$$i_x + i_1 = 0 \Rightarrow \frac{v_{OC}}{10} - 0.6v_{OC} = -0.5v_{OC} = 0.$$

The last equation certainly implies that  $v_{OC} = 0$ .

**Determination of  $R_{Th}$ :** To determine  $R_{Th}$ , we use test voltage and test current method. We apply the voltage  $v_t$  to the circuit, and compute  $i_t$  drawn by the circuit. Thus, consider Figure 1c. As before we note that

$$i_x = \frac{v_t}{10}, \quad \text{and} \quad v_1 = v_t - 16i_x = -0.6v_t.$$

Thus,

$$i_1 = \frac{v_1}{1} = -0.6v_t$$

Now the node equation at b or a implies that

$$i_t = i_x + i_1 \Rightarrow i_t = \frac{v_t}{10} - 0.6v_t = -0.5v_t.$$

Thus the Thevenin resistance  $R_{Th}$  equals  $\frac{v_t}{i_t} = -2\Omega$ .

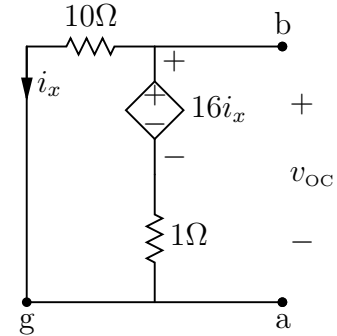


Figure 1a

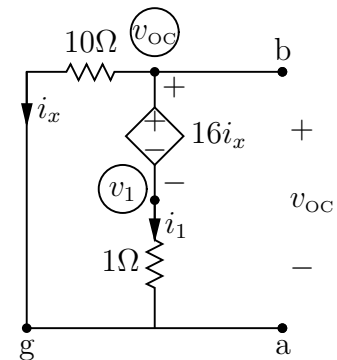


Figure 1b

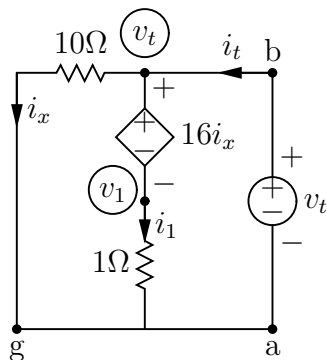


Figure 1c

**Example 2.** Determine the Thevenin equivalent circuit of two resistances  $R_1$  and  $R_2$  connected in parallel. Obviously, as there are no independent sources, the open circuit voltage is zero, and  $R_{TH} = \frac{R_1 R_2}{R_1 + R_2}$ .

**Example 3.** Determine the Thevenin equivalent circuit of an ideal battery of 12 V. Obviously, the open circuit voltage is 12 V, and  $R_{TH} = 0$ .

## Principles of Electrical Engineering I

### Maximum Power Transfer

Consider the interconnection of two circuits  $\alpha$  and  $\beta$  as shown in Figure 1. The circuit  $\alpha$  is an active circuit with sources (both independent and dependent) while the circuit  $\beta$  is a passive load on the circuit  $\alpha$ . Let the equivalent resistance of circuit  $\beta$  be  $R_L$ . Determine  $R_L$  such that power transferred by the circuit  $\alpha$  to the load  $R_L$  is maximum.

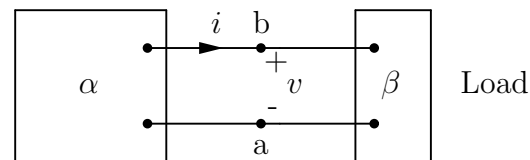


Figure 1

By replacing the circuit  $\alpha$  by its Thevenin equivalent, we can redraw the circuit of Figure 1 as that in Figure 2.

Current  $i$  is given by

$$i = \frac{v_{Th}}{R_{Th} + R_L}$$

Power consumed by  $R_L$ ,

$$P = i^2 R_L = \frac{v_{Th}^2 R_L}{(R_{Th} + R_L)^2}$$

We need to determine  $R_L$  such that  $P$  is maximum. We need to set

$$\frac{dP}{dR_L} = 0.$$

Differentiation formula,

$$d[V^{-1}U] = V^{-1}dU - V^{-2}dV U = \frac{V dU - dV U}{V^2}.$$

Applying the above rule with  $V = (R_{Th} + R_L)^2$  and  $U = R_L$ , we get

$$\begin{aligned} \frac{\partial P}{\partial R_L} &= \frac{v_{Th}^2 [(R_{Th} + R_L)^2 - 2(R_{Th} + R_L)R_L]}{(R_{Th} + R_L)^4} = 0 \\ &\Rightarrow (R_{Th} + R_L)^2 - 2(R_{Th} + R_L)R_L = 0 \Rightarrow (R_{Th} + R_L) - 2R_L = 0. \end{aligned}$$

This yields

$$R_L = R_{Th}.$$

In words, the load resistance  $R_L$  equals the Thevenin resistance ( $R_{Th}$ ) in order to maximize the power  $P$  consumed by the load.

Second derivative of  $P$  with respect to  $R_L$  confirms that  $P$  is maximum when  $R_L = R_{Th}$ . Verify yourself.

$$\text{Maximum Power} = \frac{R_{Th}}{(2R_{Th})^2} v_{Th}^2 = \frac{v_{Th}^2}{4R_{Th}}.$$

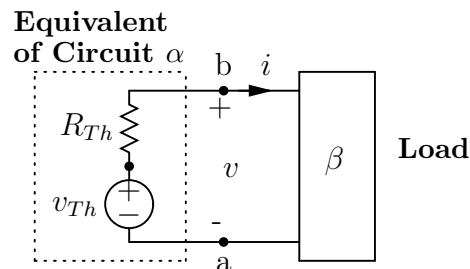


Figure 2

## HW from Nilsson and Riedel 8th and 9th editions

Set up the equations for the following problems. Solve them numerically by utilizing your calculator or Matlab.

### Nilsson and Riedel 8th edition:

4.61, 4.62

4.72 You can first develop a Thevenin equivalent to the circuit left of  $50k\Omega$ , once you do that replace the circuit left of  $50k\Omega$  by its Thevenin equivalent and then develop a Thevenin equivalent at the terminals a and b.

4.77 There are no independent sources. So, Thevenin voltage is zero. Find the Thevenin resistance by test voltage test current method.

### Nilsson and Riedel 9th edition:

4.60, 4.62

4.73 You can first develop a Thevenin equivalent to the circuit left of  $50k\Omega$ , once you do that replace the circuit left of  $50k\Omega$  by its Thevenin equivalent and then develop a Thevenin equivalent at the terminals a and b.

4.78 There are no independent sources. So, Thevenin voltage is zero. Find the Thevenin resistance by test voltage test current method.

An email will inform the due date

Name in CAPITAL LETTERS:


LAST FOUR DIGITS OF ID NUMBER:

HW: Thevenin Equivalent Circuit, 5 pages


332:221 Principles of Electrical Engineering I

This problem will be collected and graded.

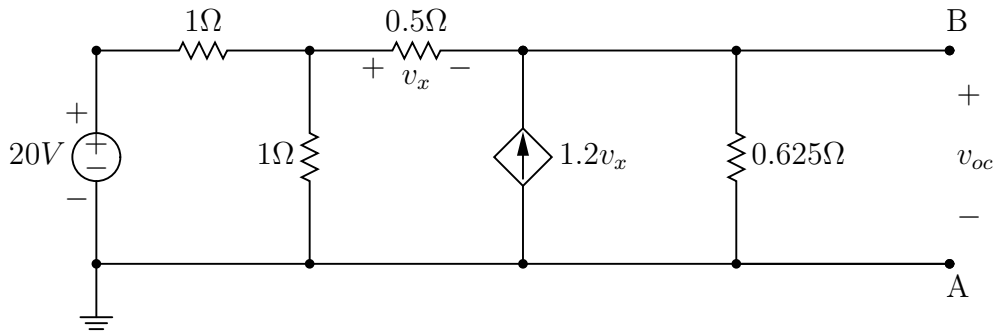
(Problem 1a) Determination of  $v_{Th} = v_{oc}$  by node voltage method: Consider the circuit shown below. Our aim in this problem is to determine the open circuit voltage  $v_{oc}$  at the terminals A and B by utilizing the node voltage method. Consider the grounded terminal as the reference node.



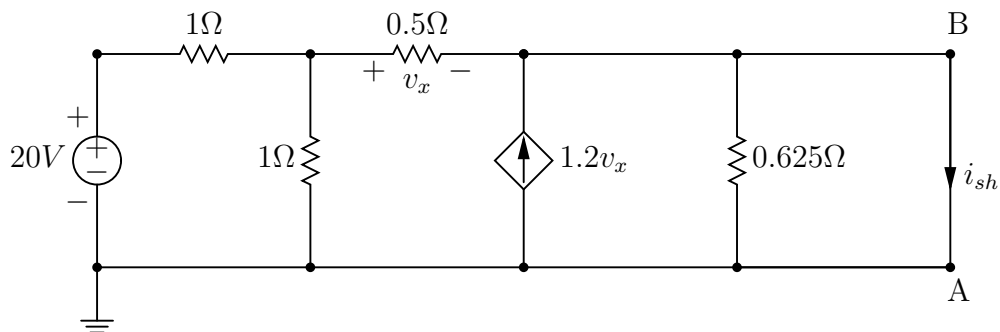
**(Problem 1b) Determination of  $i_{sh}$  by node voltage method:** Consider the circuit shown below. Our aim in this problem is to determine the short circuit current  $i_{sh}$  through the terminals A and B by utilizing the node voltage method. Consider the grounded terminal as the reference node.



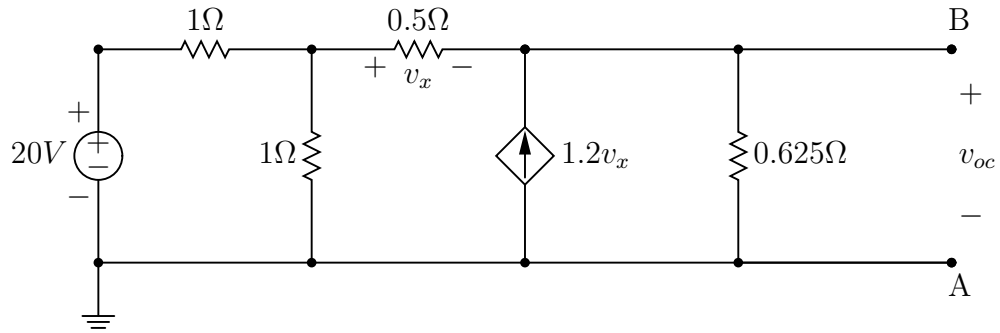**(Problem 1c) Determination of  $v_{Th} = v_{oc}$  by mesh current method:** Consider the circuit shown below. Our aim in this problem is to determine the open circuit voltage  $v_{oc}$  at the terminals A and B by utilizing the mesh current method.




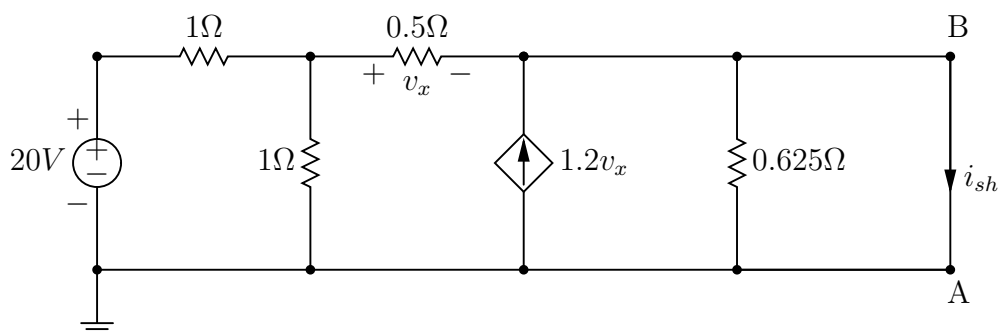**(Problem 1d) Determination of  $i_{sh}$  by mesh current method:** Consider the circuit shown below. Our aim in this problem is to determine the short circuit current  $i_{sh}$  through the terminals A and B by utilizing the mesh current method.





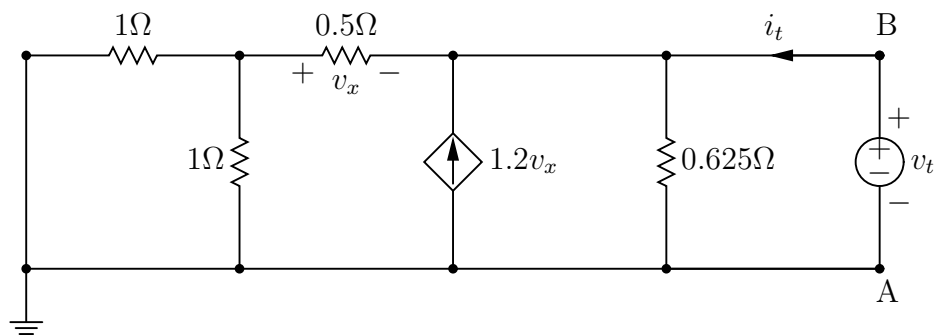**(Problem 1e) Determination of  $R_{Th}$  by test voltage and test current method:** We first construct an independent source-less circuit. Apply a test voltage  $v_t$  at the terminals A and B, and determine the test current  $i_t$  supplied by it to the circuit. Then we recognize that the Thevenin resistance  $R_{Th}$  is the ratio  $\frac{v_t}{i_t}$ . Utilize any method to determine the ratio  $\frac{v_t}{i_t}$ . The independent source-less circuit along with the test source is as shown below.



Name in CAPITAL LETTERS:  
 LAST FOUR DIGITS OF ID NUMBER:

HW: DAC Thevenin Equivalent

332:221 Principles of Electrical Engineering I

Theme Example – DAC– Thevenin equivalent circuit at the output terminals  
 HW, collected and graded

Digital  
 to analog  
 converter  
 (DAC)  
 circuit.

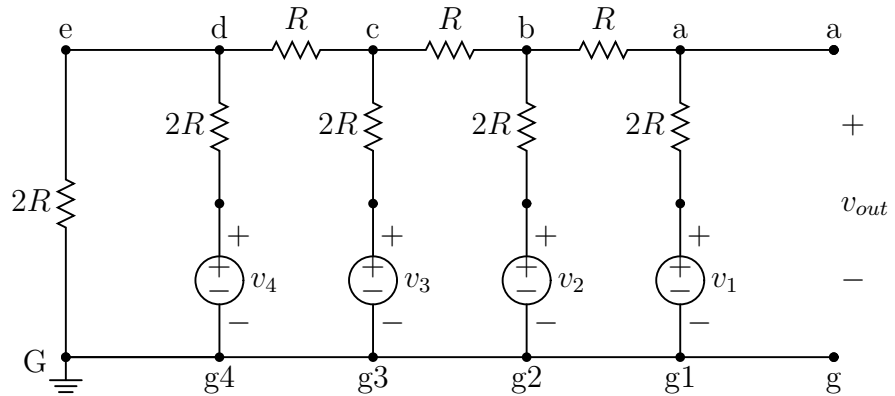


Figure 1

Determination of the Thevenin equivalent circuit at the output terminals ‘g’ and ‘a’:

Thevenin voltage  $v_{Th}$  is the open circuit voltage at the output terminals ‘g’ and ‘a’. That is, it is the output voltage  $v_{out}$  when no load is connected at the terminals ‘g’ and ‘a’ as in Figure 1. Such a voltage has been determined as (you need not show this),

$$v_{Th} = \frac{1}{2}v_1 + \frac{1}{4}v_2 + \frac{1}{8}v_3 + \frac{1}{16}v_4.$$

Thevenin resistance  $R_{Th}$  is the same as the resistance  $R_{Th}$  seen from the output terminals ‘g’ and ‘a’ as shown in Figure 1R where all the source voltages  $v_1, v_2, v_3,$  and  $v_4$  are set to zero. Determine Thevenin resistance  $R_{Th}$ .


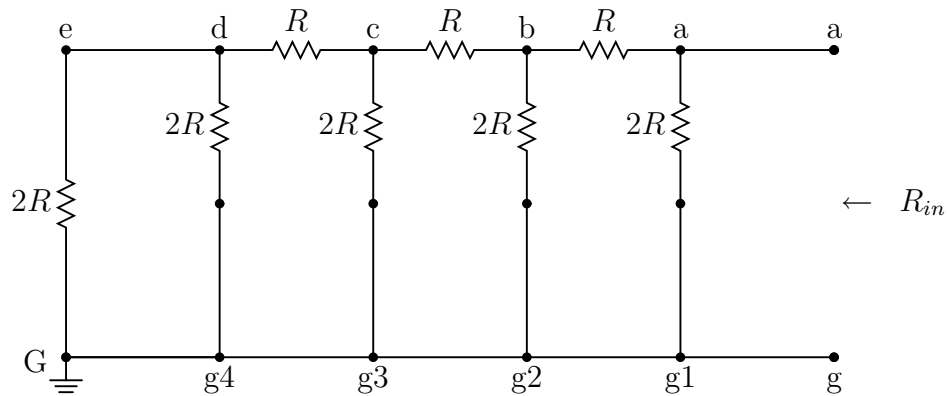


Figure 1R

Draw below the Thevenin equivalent circuit at the output terminals ‘g’ and ‘a’.

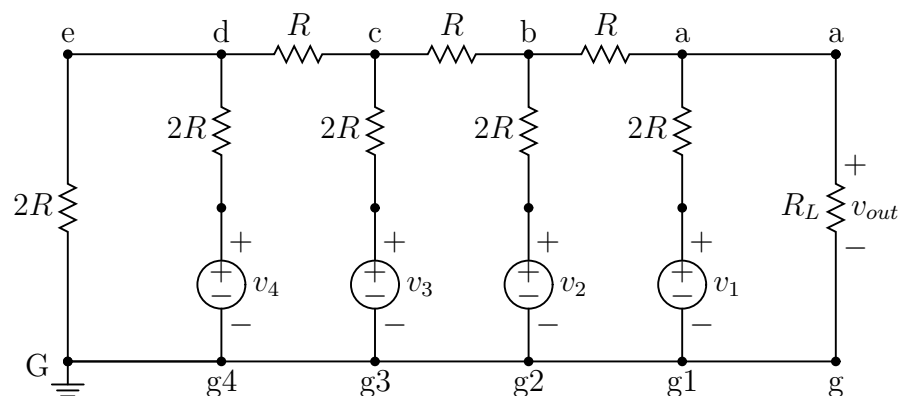**Determination of  $v_{out}$  when a load  $R_L$  is connected at the output terminals 'g' and 'a':**  
 Connect a load of  $R_L$  at the output terminals 'g' and 'a' as shown below.



Modify the Thevenin equivalent circuit drawn earlier to include the load, then determine the resulting output voltage  $v_{out}$ . Note that  $v_{out}$  is a function of  $R_L$ . This implies that the load affects the output voltage  $v_{out}$ . **We will see later on how to avoid this.**