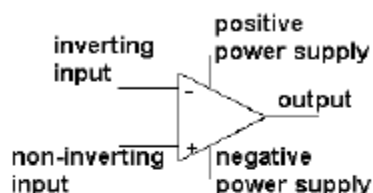


Subject: ECE221 Fall'12 PS 6 Solution**From:** Christopher Rose <crose@winlab.rutgers.edu>**Date:** 10/03/2012 03:34 PM**To:** Christopher Rose <crose@winlab.rutgers.edu>

ECE221 Fall'12 PS 6 Solution

(5.1, 5.6, 5.9, 5.13, 5.16, 5.27, 5.34, 5.41)

P 5.1 [a] The five terminals of the op amp are identified as follows:



- [b] The input resistance of an ideal op amp is infinite, which constrains the value of the input currents to 0. Thus, $i_n = 0$ A.
- [c] The open-loop voltage gain of an ideal op amp is infinite, which constrains the difference between the voltage at the two input terminals to 0. Thus, $(v_p - v_n) = 0$.
- [d] Write a node voltage equation at v_n :

$$\frac{v_n + 3}{5000} + \frac{v_n - v_o}{15,000} = 0$$

But $v_p = 0$ and $v_n = v_p = 0$. Thus,

$$\frac{3}{5000} - \frac{v_o}{15,000} = 0 \quad \text{so} \quad v_o = 9 \text{ V}$$

P 5.6 [a] $i_2 = \frac{150 \times 10^{-3}}{2000} = 75 \mu\text{A}$

$$v_1 = -40 \times 10^3 i_2 = -3 \text{ V}$$


[b] $\frac{v_1}{20,000} + \frac{v_1}{40,000} + \frac{v_1 - v_o}{50,000} = 0$

$$\therefore v_o = 4.75 v_1 = -14.25 \text{ V}$$

[c] $i_2 = 75 \mu\text{A}$, (from part [a])

[d] $i_o = \frac{-v_o}{25,000} + \frac{v_1 - v_o}{50,000} = 795 \mu\text{A}$

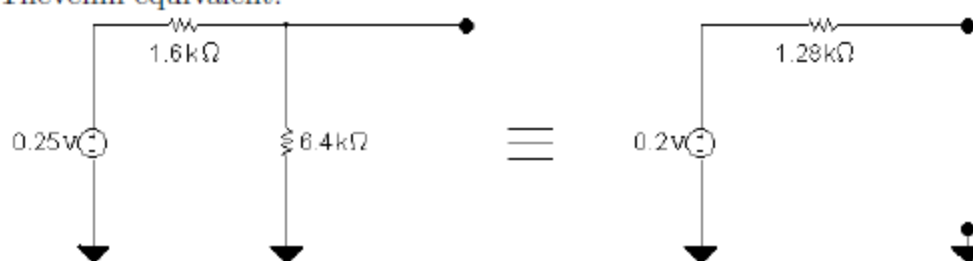- P 5.9 [a] Replace the combination of v_g , $1.6\text{ k}\Omega$, and the $6.4\text{ k}\Omega$ resistors with its Thévenin equivalent.



$$\text{Then } v_o = \frac{-(12 + \sigma 50)}{1.28}(0.20)$$

At saturation $v_o = -5\text{ V}$; therefore

$$-\left(\frac{12 + \sigma 50}{1.28}\right)(0.2) = -5, \quad \text{or } \sigma = 0.4$$

Thus for $0 \leq \sigma \leq 0.40$ the operational amplifier will not saturate.

[b] When $\sigma = 0.272$, $v_o = \frac{-(12 + 13.6)}{1.28}(0.20) = -4\text{ V}$

$$\text{Also } \frac{v_o}{10} + \frac{v_o}{25.6} + i_o = 0$$

$$\therefore i_o = -\frac{v_o}{10} - \frac{v_o}{25.6} = \frac{4}{10} + \frac{4}{25.6}\text{ mA} = 556.25\text{ }\mu\text{A}$$

P 5.13 We want the following expression for the output voltage:

$$v_o = -(3v_a + 5v_b + 4v_c + 2v_d)$$

This is an inverting summing amplifier, so each input voltage is amplified by a gain that is the ratio of the feedback resistance to the resistance in the forward path for the input voltage. Pick a feedback resistor with divisors of 3, 5, 4, and 2 – say $60\text{ k}\Omega$:


$$v_o = -\left[\frac{60\text{k}}{R_a}v_a + \frac{60\text{k}}{R_b}v_b + \frac{60\text{k}}{R_c}v_c + \frac{60\text{k}}{R_d}v_d\right]$$

Solve for each input resistance value to yield the desired gain:

$$\therefore R_a = 60,000/3 = 20\text{ k}\Omega \quad R_c = 60,000/4 = 15\text{ k}\Omega$$

$$R_b = 60,000/5 = 12\text{ k}\Omega \quad R_d = 60,000/2 = 30\text{ k}\Omega$$

Now create the 5 resistor values needed from the realistic resistor values in Appendix H. Note that $R_b = 12\text{ k}\Omega$ and $R_c = 15\text{ k}\Omega$ are already values from Appendix H. Create $R_f = 60\text{ k}\Omega$ by combining $27\text{ k}\Omega$ and $33\text{ k}\Omega$ in series. Create $R_a = 20\text{ k}\Omega$ by combining two $10\text{ k}\Omega$ resistors in series. Create $R_d = 30\text{ k}\Omega$ by combining $18\text{ k}\Omega$ and $12\text{ k}\Omega$ in series. Of course there are many other acceptable possibilities. The final circuit is shown here:

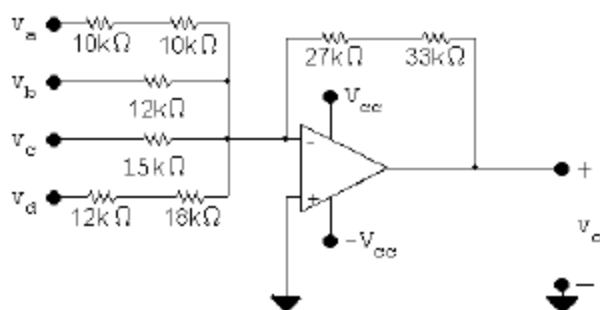

P 5.16 [a] The circuit shown is a non-inverting amplifier.

[b] We assume the op amp to be ideal, so $v_n = v_p = 3\text{ V}$. Write a KCL equation at v_n :

$$\frac{3}{40,000} + \frac{3 - v_o}{80,000} = 0$$

Solving,

$$v_o = 9\text{ V}.$$

$$\text{P 5.27} \quad v_p = \frac{v_b R_b}{R_a + R_b} = v_n$$

$$\frac{v_n - v_a}{4700} + \frac{v_n - v_o}{R_f} = 0$$

$$v_n \left(\frac{R_f}{4700} + 1 \right) - \frac{v_a R_f}{4700} = v_o$$

$$\therefore \left(\frac{R_f}{4700} + 1 \right) \frac{R_b}{R_a + R_b} v_b - \frac{R_f}{4700} v_a = v_o$$

$$\therefore \frac{R_f}{4700} = 10; \quad R_f = 47 \text{ k}\Omega \quad (\text{a value from Appendix H})$$

$$R_a + R_b = 220 \text{ k}\Omega$$

Thus,

$$\left(1 + \frac{47}{4700} \right) \left(\frac{R_b}{220,000} \right) = 10$$

$$\therefore R_b = 200 \text{ k}\Omega \quad \text{and} \quad R_a = 220 - 200 = 20 \text{ k}\Omega$$


Use two 100 k Ω resistors in series for R_b and use two 10 k Ω resistors in series for R_a .

$$\text{P 5.34} \quad [\text{a}] \quad A_{\text{dm}} = \frac{(24)(26) + (25)(25)}{(2)(1)(25)} = 24.98$$

$$[\text{b}] \quad A_{\text{cm}} = \frac{(1)(24) - 25(1)}{1(25)} = -0.04$$

$$[\text{c}] \quad \text{CMRR} = \left| \frac{24.98}{0.04} \right| = 624.50$$

P 5.41

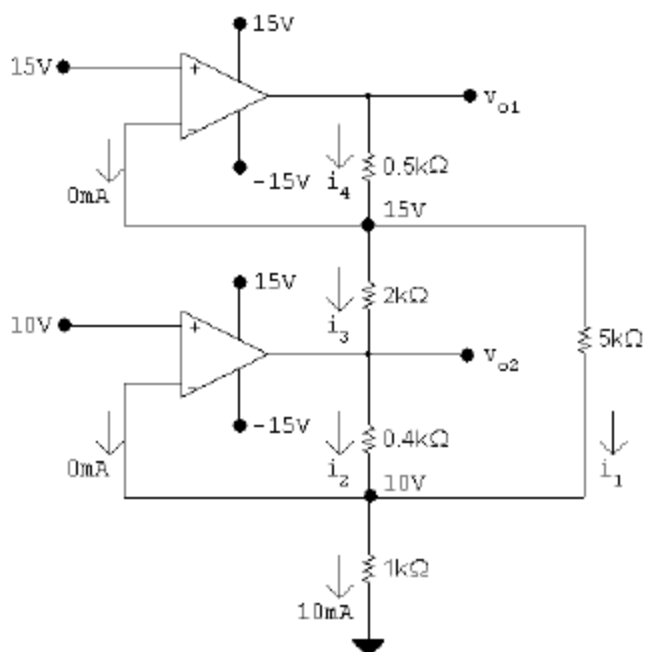

$$i_1 = \frac{15 - 10}{5000} = 1 \text{ mA}$$

$$i_2 + i_1 + 0 = 10 \text{ mA}; \quad i_2 = 9 \text{ mA}$$

$$v_{o2} = 10 + (400)(9) \times 10^{-3} = 13.6 \text{ V}$$

$$i_3 = \frac{15 - 13.6}{2000} = 0.7 \text{ mA}$$

$$i_4 = i_3 + i_1 = 1.7 \text{ mA}$$

$$v_{o1} = 15 + 1.7(0.5) = 15.85 \text{ V}$$