
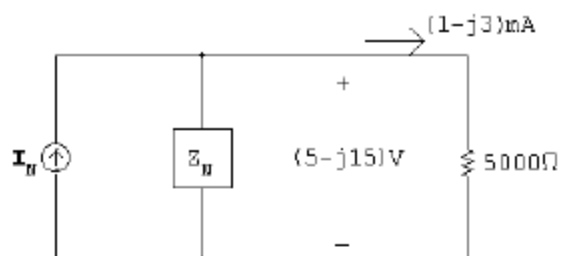


ECE221 Problem Set 9 Solutions (9.43, 9.48, 9.56, 9.59, 9.62, 9.64, 9.71, 9.84, 9.87)

P 9.43

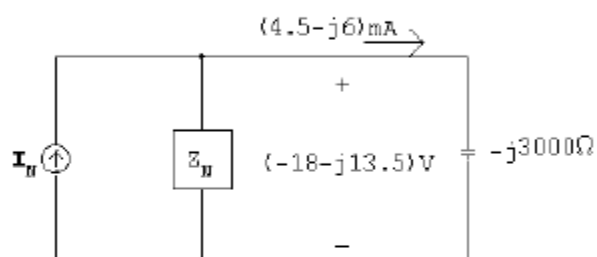

$$\mathbf{I}_N = \frac{5 - j15}{Z_N} + (1 - j3) \text{ mA}, \quad Z_N \text{ in } \text{k}\Omega$$




$$\mathbf{I}_N = \frac{-18 - j13.5}{Z_N} + 4.5 - j6 \text{ mA}, \quad Z_N \text{ in } \text{k}\Omega$$


$$\frac{5 - j15}{Z_N} + 1 - j3 = \frac{-18 - j13.5}{Z_N} + (4.5 - j6)$$

$$\frac{23 - j15}{Z_N} = 3.5 - j3 \quad \therefore \quad Z_N = 4 + j3 \text{ k}\Omega$$
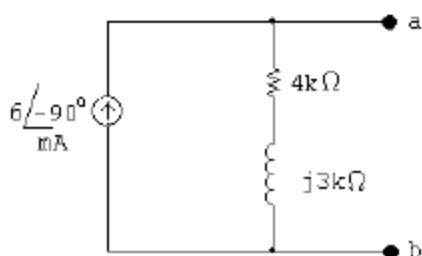
$$\mathbf{I}_N = \frac{5 - j15}{4 + j3} + 1 - j3 = -j6 \text{ mA}$$



P 9.48 Open circuit voltage:

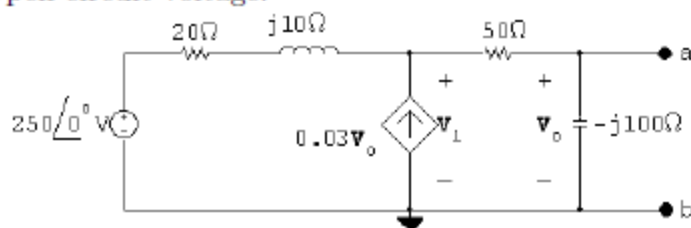


$$\frac{V_1 - 250}{20 + j10} - 0.03V_o + \frac{V_1}{50 - j100} = 0$$

$$\therefore V_o = \frac{-j100}{50 - j100} V_1$$

$$\frac{V_1}{20 + j10} + \frac{j3V_1}{50 - j100} + \frac{V_1}{50 - j100} = \frac{250}{20 + j10}$$

$$V_1 = 500 - j250 \text{ V}; \quad V_o = 300 - j400 \text{ V} = V_{Th}$$


Short circuit current:

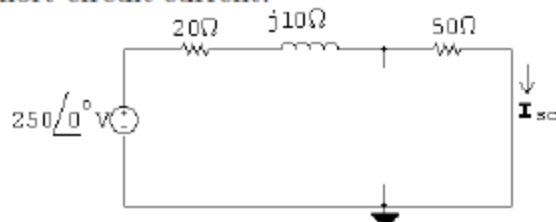


$$I_{sc} = \frac{250\angle 0^\circ}{70 + j10} = 3.5 - j0.5 \text{ A}$$

$$Z_{Th} = \frac{V_{Th}}{I_{sc}} = \frac{300 - j400}{3.5 - j0.5} = 100 - j100 \Omega$$

The Thévenin equivalent circuit:

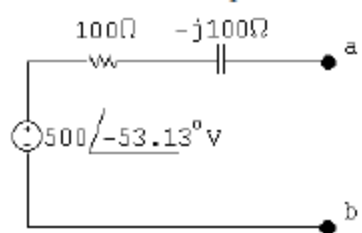

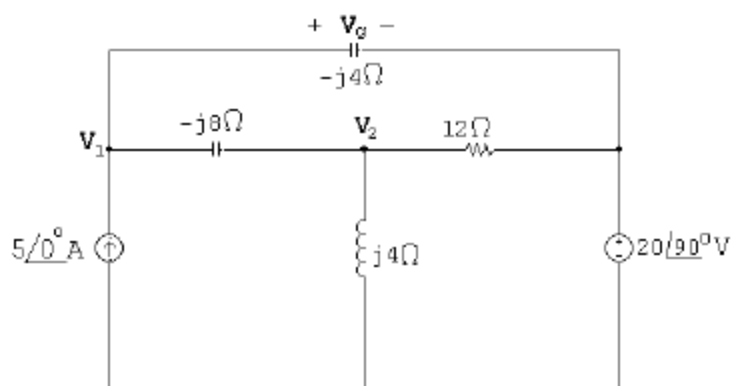P 9.56 Set up the frequency domain circuit to use the node voltage method:



$$\text{At } \mathbf{V}_1: \quad -5\angle 0^\circ + \frac{\mathbf{V}_1 - \mathbf{V}_2}{-j8} + \frac{\mathbf{V}_1 - 20\angle 90^\circ}{-j4} = 0$$

$$\text{At } \mathbf{V}_2: \quad \frac{\mathbf{V}_2 - \mathbf{V}_1}{-j8} + \frac{\mathbf{V}_2}{j4} + \frac{\mathbf{V}_2 - 20\angle 90^\circ}{12} = 0$$

In standard form:

$$\mathbf{V}_1 \left(\frac{1}{-j8} + \frac{1}{-j4} \right) + \mathbf{V}_2 \left(-\frac{1}{-j8} \right) = 5\angle 0^\circ + \frac{20\angle 90^\circ}{-j4}$$

$$\mathbf{V}_1 \left(-\frac{1}{-j8} \right) + \mathbf{V}_2 \left(\frac{1}{-j8} + \frac{1}{j4} + \frac{1}{12} \right) = \frac{20\angle 90^\circ}{12}$$

Solving on a calculator:

$$\mathbf{V}_1 = -\frac{8}{3} + j\frac{4}{3} \quad \mathbf{V}_2 = -8 + j4$$

Thus

$$\mathbf{V}_g = \mathbf{V}_1 - 20\angle 90^\circ = -\frac{8}{3} - j\frac{56}{3} \text{ V}$$

P 9.59 Write a KCL equation at the top node:

$$\frac{\mathbf{V}_o}{-j8} + \frac{\mathbf{V}_o - 2.4\mathbf{I}_\Delta}{j4} + \frac{\mathbf{V}_o}{5} - (10 + j10) = 0$$


The constraint equation is:

$$\mathbf{I}_\Delta = \frac{\mathbf{V}_o}{-j8}$$

Solving,

$$\mathbf{V}_o = j80 = 80/\underline{90^\circ} \text{ V}$$

P 9.62

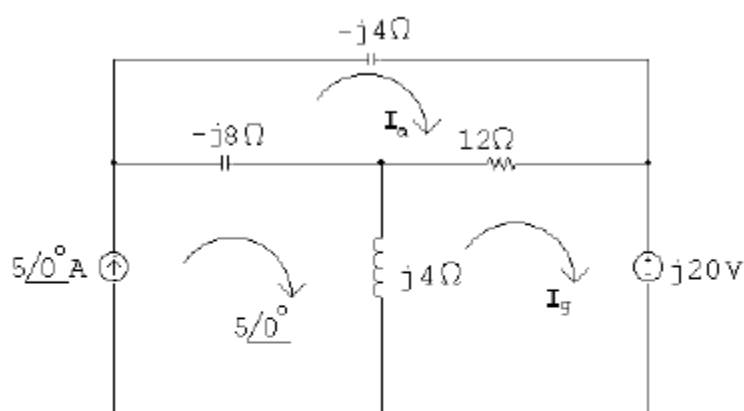

$$(12 - j12)\mathbf{I}_a - 12\mathbf{I}_g - 5(-j8) = 0$$


$$-12\mathbf{I}_a + (12 + j4)\mathbf{I}_g + j20 - 5(j4) = 0$$

Solving,

$$\mathbf{I}_g = 4 - j2 = 4.47/\underline{-26.57^\circ} \text{ A}$$

P 9.64 $j\omega L = j10,000(5 \times 10^{-3}) = j50 \Omega$
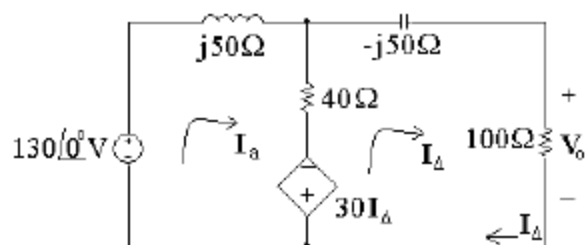
$$\frac{1}{j\omega C} = \frac{-j}{(10,000)(2 \times 10^{-6})} = -j50 \Omega$$



$$130\angle 0^\circ = (40 + j50)\mathbf{I}_a - 40\mathbf{I}_\Delta + 30\mathbf{I}_\Delta$$

$$0 = -40\mathbf{I}_a + 30\mathbf{I}_\Delta + (140 - j50)\mathbf{I}_\Delta$$

Solving,

$$\mathbf{I}_\Delta = (400 - j400) \text{ mA}$$

$$\mathbf{V}_o = 100\mathbf{I}_\Delta = 40 - j40 = 56.57\angle -45^\circ$$

$$v_o = 56.57 \cos(10,000t - 45^\circ) \text{ V}$$

P 9.71 [a] $\frac{1}{j\omega C} = \frac{-j10^9}{(10^6)(10)} = -j100 \Omega$

$$V_g = 30\angle 0^\circ \text{ V}$$

$$V_p = \frac{V_g(1/j\omega C_o)}{25 + (1/j\omega C_o)} = \frac{30\angle 0^\circ}{1 + j25\omega C_o} = V_n$$

$$\frac{V_n}{100} + \frac{V_n - V_o}{-j100} = 0$$

$$V_o = \frac{1 + j1}{j} V_n = (1 - j1)V_n = \frac{30(1 - j1)}{1 + j25\omega C_o}$$

$$|V_o| = \frac{30\sqrt{2}}{\sqrt{1 + 625\omega^2 C_o^2}} = 6$$


Solving,

$$C_o = 280 \text{ nF}$$

[b] $V_o = \frac{30(1 - j1)}{1 + j7} = 6\angle -126.87^\circ$


$$v_o = 6 \cos(10^6 t - 126.87^\circ) \text{ V}$$

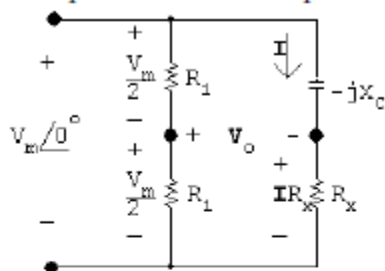P 9.84 The phasor domain equivalent circuit is



$$V_o = \frac{V_m}{2} - IR_x; \quad I = \frac{V_m}{R_x - jX_C}$$

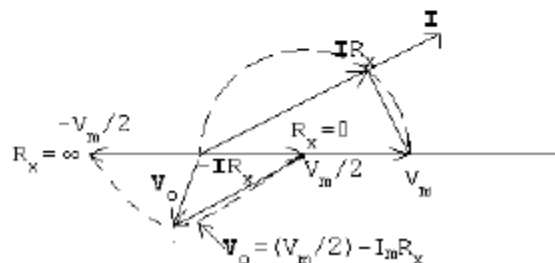As R_x varies from 0 to ∞ , the amplitude of v_o remains constant and its phase angle increases from 0° to -180° , as shown in the following phasor diagram:



1

$$\text{P 9.87 [a] } \mathbf{I}_1 = \frac{120}{24} + \frac{240}{8.4 + j6.3} = 23.29 - j13.71 = 27.02/\underline{-30.5^\circ} \text{ A}$$

$$\mathbf{I}_2 = \frac{120}{12} - \frac{120}{24} = 5/\underline{0^\circ} \text{ A}$$

$$\mathbf{I}_3 = \frac{120}{12} + \frac{240}{8.4 + j6.3} = 28.29 - j13.71 = 31.44/\underline{-25.87^\circ} \text{ A}$$

$$\mathbf{I}_4 = \frac{120}{24} = 5/\underline{0^\circ} \text{ A}; \quad \mathbf{I}_5 = \frac{120}{12} = 10/\underline{0^\circ} \text{ A}$$

$$\mathbf{I}_6 = \frac{240}{8.4 + j6.3} = 18.29 - j13.71 = 22.86/\underline{-36.87^\circ} \text{ A}$$

[b] When fuse A is interrupted,

$$\mathbf{I}_1 = 0 \qquad \mathbf{I}_3 = 15 \text{ A} \qquad \mathbf{I}_5 = 10 \text{ A}$$

$$\mathbf{I}_2 = 10 + 5 = 15 \text{ A} \qquad \mathbf{I}_4 = -5 \text{ A} \qquad \mathbf{I}_6 = 5 \text{ A}$$

[c] The clock and television set were fed from the uninterrupted side of the circuit, that is, the 12Ω load includes the clock and the TV set.

[d] No, the motor current drops to 5 A, well below its normal running value of 22.86 A.

[e] After fuse A opens, the current in fuse B is only 15 A.

--

```
*****
* Prof. Christopher Rose *
* Rutgers Electrical & Computer Eng. *
* WINLAB *
* Technology Center of New Jersey *
* 671 Route 1 South *
* North Brunswick, NJ 08902-3390 *
* voice: 732-932-6857 x643 *
* 732-932-6882 (Fax) *
* http://www.winlab.rutgers.edu/~crose *
*****
```