



RUTGERS

School of Engineering
Department of Electrical and Computer Engineering


332:221

Principles of Electrical Engineering I
Quizlette 10

Fall 2012

USING A CALCULATOR WILL SLOW YOU DOWN! Final answers must appear in the appropriate box. Show your work outside the box.

1. **Basic Stuff:**

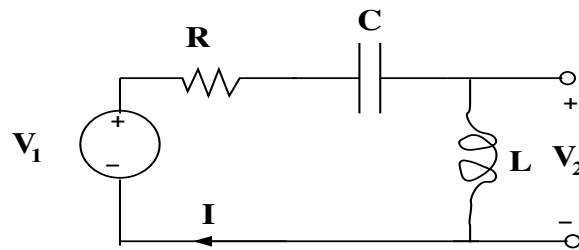

Assume sinusoidal steady state operation at some frequency ω and suppose $V_1 = V e^{j\theta}$ and $I = I e^{j\phi}$.

(a) (1 pts) What is the maximum value (amplitude) of the input voltage $V_1(t)$?

V

(b) (1 pts) What is the RMS value of the input voltage $V_1(t)$?

$\{V_1(t)\}_{RMS} = \frac{V}{\sqrt{2}}$


(c) (1 pts) Which is larger, $\max_t V_1(t)$ or $\{V_1(t)\}_{RMS}$

V_{RMS} is smaller.

(d) (2 pts) What is the average power *supplied to* the resistor, capacitor and inductor?

$$\overline{P} = \frac{1}{2} \mathbf{V} \mathbf{I}^* = \frac{VI}{2} \Re\{e^{j(\theta-\phi)}\} = \frac{VI}{2} \cos(\theta - \phi)$$

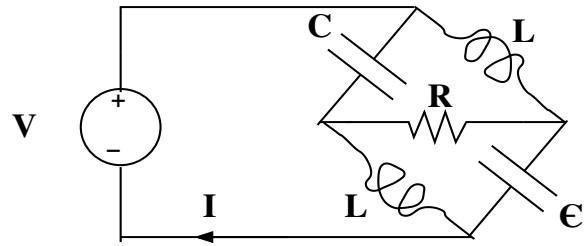2. **VERY Cute:** Assume sinusoidal steady state at some frequency ω .



- (a) (2 pt) Assume $\mathbf{V} = V e^{j\theta}$ and $\mathbf{I} = I e^{j\theta}$. What is the amplitude of the voltage across the resistor?

$$\frac{V_R^2}{R} == \Re\{V I^*\} = V I \text{ so } V_R = \sqrt{R V I}$$

- (b) (3 pts) At what value of ω (if any) does V_R , the voltage across the resistor, equal zero?

When the bridge is balanced:

$$\frac{1}{1 - LC\omega^2} = \frac{-LC\omega^2}{1 - LC\omega^2}$$

implies

$$LC\omega^2 = -1$$

which is impossible.