

NAME:

LAB SECTION:



# RUTGERS

School of Engineering  
Department of Electrical and Computer Engineering


332:221

Principles of Electrical Engineering I  
Quizlette 11

Fall 2012

*USING A CALCULATOR WILL SLOW YOU DOWN! Final answers must appear in the appropriate box.  
Show your work outside the box.*

1. Basic Then ... Not Basic:

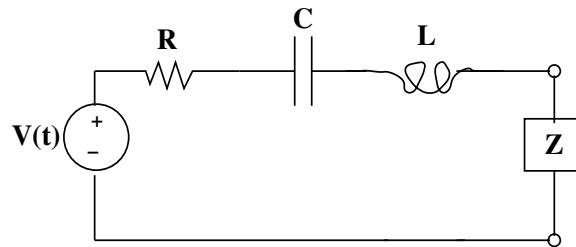


Assume sinusoidal steady state operation at some frequency  $\omega$ .

- (a) (2pts) What value of  $Z$  maximizes the average power transferred to  $Z$ ?

- (b) (3 pts) Suppose we require  $Z = R_L$  to be real (i.e., just a regular old resistor). What value of  $R_L$  maximizes power transfer into  $Z$ ?

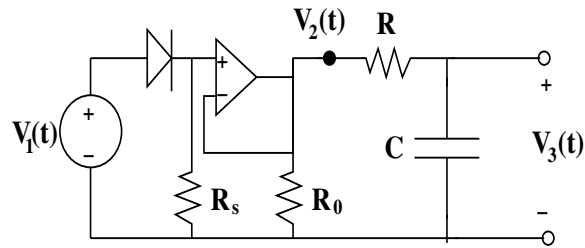2. **Your Cute Future:** Consider the circuit shown in the figure.



- (a) (1 pt) Assume the input voltage source amplitude is  $V_1 = V_1$  where  $V_1 \in \mathbb{R}$  and that the frequency of operation is  $\omega$ . Please provide a labeled sketch of  $V_2(t)$ .

- (b) (1 pts) Can you provide a transfer function from  $V_1$  to  $V_3$ ? Why?/Why not?

- (c) (1 pts) If  $\omega = 2\pi \cdot 60$  and  $R = 10k\Omega$ , provide (and argue for) a value of  $C$  that makes  $V_3(t) \approx V_1$ ? **HINT:** Remember that  $RC$  is called the “time constant” and is a measure of how quickly charge bleeds from a capacitor  $C$  through a resistor  $R$ .

- (d) (2 pts) You are told that

$$V_2(t) = V_1 \sum_{k=-\infty}^{\infty} \frac{\cos \frac{k\pi}{2}}{\pi(1 - k^2)} e^{jk\omega t}$$

is the analytic form of what you SHOULD have sketched in the previous part :) :) . What is the output  $V_3(t)$ .