



# RUTGERS

School of Engineering  
Department of Electrical and Computer Engineering

332:221

## Principles of Electrical Engineering I Quizlette 3

Fall 2012

**USING A CALCULATOR WILL SLOW YOU DOWN! Final answers must appear in the appropriate box. Show your work outside the box.**

1. **Basic Stuff:** Please answer the following questions about FIGURE 1.

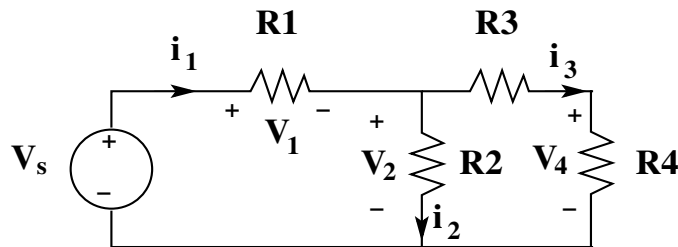


Figure 1: Circuit diagram for problem 1

- (a) (1 pt) (TRUE/FALSE)  $R3$  is in series with  $R4$ :

**T**

- (b) (1 pt) (TRUE/FALSE)  $R2$  is in parallel with  $R4$ :

**F**

- (c) (1 pt) What is  $V_2$  in terms of  $i_1$ ,  $R2$ ,  $R3$  and  $R4$ ?

$$V_2 = i_1 R_2 \frac{R_3 + R_4}{R_2 + R_3 + R_4}$$

- (d) (2 pts) If  $R1 = R3 = R4 = 1$  and  $R2 = 2$ , what is  $i_1$  in terms of  $V_s$ ?

$$i_1 = V_s / 2$$

## 2. Getting Cute:

For the two-port network shown in FIGURE 2(a), you are told

$$V_1 = H_{11}I_1 + H_{21}I_2$$

$$V_2 = H_{12}I_1 + H_{22}I_2$$

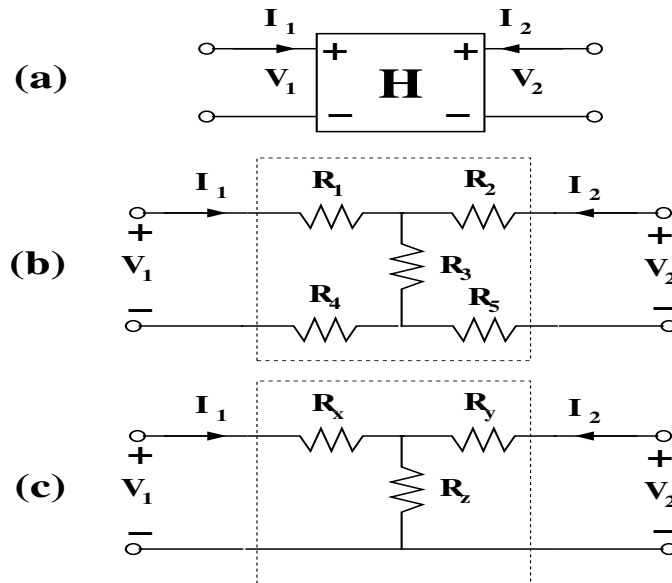


Figure 2: Circuit diagrams for problem 2

- (a) (1 pt) What is  $H_{11}$  in terms of the resistance values in FIGURE 2(b).

$$H_{11} = R_1 + R_3 + R_4$$

- (b) (1 pt) What is  $H_{22}$  in terms of the resistance values in FIGURE 2(b)?

$$H_{22} = R_2 + R_3 + R_5$$

- (c) (1 pt) What are  $H_{12}$  and  $H_{21}$  in terms of the resistance values in FIGURE 2(b)?

$$H_{12} = H_{21} = R_3$$

- (d) (2 pts) Please find values of  $R_x$ ,  $R_y$  and  $R_z$  in FIGURE 2(c) in terms of  $R_n$ ,  $n = 1, \dots, 5$  in FIGURE 2(b) that make the two circuits equivalent.

$$\begin{aligned} R_z &= R_3. \text{ Then,} \\ R_x + R_z &= R_1 + R_3 + R_4 \\ \text{so } R_x &= R_1 + R_4. \\ \text{Also, } R_y + R_z &= R_2 + R_3 + R_5 \text{ so} \\ R_y &= R_2 + R_5 \end{aligned}$$