



# RUTGERS

School of Engineering  
Department of Electrical and Computer Engineering

332:221

**Principles of Electrical Engineering I**  
Quizlette 5

Fall 2012

*USING A CALCULATOR WILL SLOW YOU DOWN! Final answers must appear in the appropriate box.  
Show your work outside the box.*

NAME:

LAB SECTION:

1. **Basic Stuff:** Please answer the following questions about FIGURE 1.

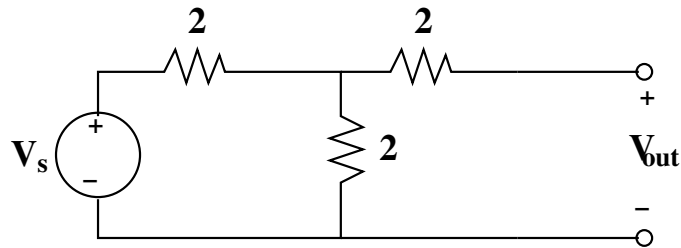


Figure 1: Circuit diagram for problem 1

- (a) (1 pt) What is the effective resistance of the circuit from the perspective of  $V_{out}$ ?
- (b) (2 pt) Draw and label the Thevenin Equivalent for the circuit.

- (c) (2 pt) Draw and label the Norton Equivalent for the circuit.

2. Getting VERY Cute:

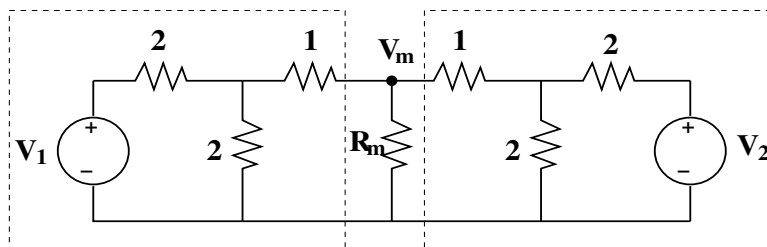


Figure 2: Circuit diagram for problem 2

- (a) (2 pts) Draw and label a Thevenin Equivalent circuit for each dashed box.

- (b) (2 pts) What is the voltage,  $V_m$ , across resistor  $R_m$ ?

- (c) (1 pts) What value of  $R_m$  maximizes the power absorbed by  $R_m$ ?