

NAME:

LAB SECTION:



RUTGERS

School of Engineering
Department of Electrical and Computer Engineering

332:221


Principles of Electrical Engineering I

Fall 2012

Quizlette 8

USING A CALCULATOR WILL SLOW YOU DOWN! Final answers must appear in the appropriate box.
Show your work outside the box.

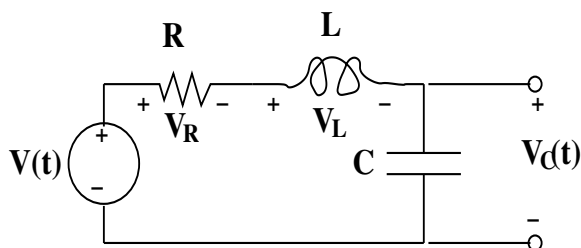1. **Basic Stuff:** The differential equation that relates $V(t)$ to $V_C(t)$ is



$$V_C + LC \frac{d^2 V_C}{dt^2} + RC \frac{dV_C}{dt} = V(t)$$

- (a) (2 pts) What is the transfer function $H(j\omega)$ between input $V(t)$ and output $V_C(t)$?

- (b) (2 pts) Suppose $V(t) = \cos t$ and all transients have died out of the circuit. Assuming $R = C = L = 1$ (in appropriate units), what is:

- i. (1 pts) the phasor form of the transfer function value?

- ii. (1 pts) $V_C(t)$?

2. Still Basic:

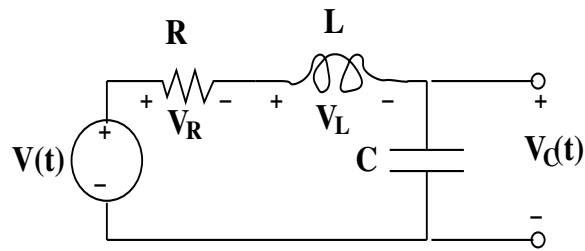


Figure 1:

(a) (2 pt)

Please derive the differential equation that relates input voltage $V(t)$ to the current $I_L(t)$ through the inductor.

(b) (2 pts) What is the transfer function $H(j\omega)$ between input $V(t)$ and output $I_L(t)$?

(c) (1 pts) Suppose $V(t) = \cos t$ and all transients have died out of the circuit. Assuming $R = C = L = 1$ (in appropriate units), what is $I_L(t)$?