



RUTGERS

School of Engineering
Department of Electrical and Computer Engineering


332:221

Principles of Electrical Engineering I
Quizlette 9

Fall 2012

**USING A CALCULATOR WILL SLOW YOU DOWN! Final answers must appear in the appropriate box.
Show your work outside the box.**

1. Basic Stuff:

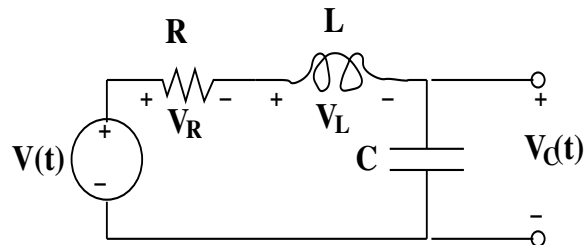

- (a) (1 pts) What is the Thevenin impedance at frequency ω for the circuit shown?

$$Z_{th} = \frac{(R+Lj\omega) \frac{1}{Cj\omega}}{R+Lj\omega + \frac{1}{Cj\omega}} = \frac{R+Lj\omega}{RCj\omega + LC(j\omega)^2 + 1}$$

- (b) (2 pts) Use impedance methods to derive the transfer function $H(j\omega)$ between input $V(t)$ and output $V_L(t)$, the voltage across the inductor as labeled .

$$H(j\omega) = \frac{Lj\omega}{R+Lj\omega + \frac{1}{Cj\omega}} = \frac{LC(j\omega)^2}{RCj\omega + LC(j\omega)^2 + 1}$$

- (c) (2 pts) The transfer function between the input voltage and the current through the capacitor, $I_C(t)$, is

$$H(j\omega) = \frac{Cj\omega}{1 + RCj\omega + LC(j\omega)^2}$$

Please write down the differential equation that relates $V(t)$ to $I_C(t)$.

$$C \frac{dV}{dt} = I_C + RC \frac{dI_C}{dt} + LC \frac{d^2 I_C}{dt^2}$$

2. Getting Cute:

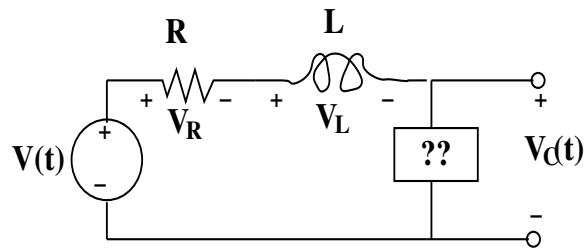


Figure 1:

- (a) (3 pt) The transfer function between input $V(t)$ and output $V_C(t)$ is

$$H(j\omega) = \frac{LC(j\omega)^2 + RCj\omega + 1}{2LC(j\omega)^2 + 2RCj\omega + 1}$$

Please find $Z_{??}$.

$$Z_{??} = Lj\omega + R + \frac{1}{Cj\omega}$$

- (b) (2 pts) You are told that the mystery box ?? contains ideal resistors, capacitors and inductors and that for input $V(t) = 10 \cos \omega t$ we have $V_C(t) = 2 \cos(\omega t - \phi_1) + 3 \sin(\omega t + \phi_2) - 4 \sin(\alpha \omega t)$ where ϕ_1 and ϕ_2 are known constant phase offsets and α is a real constant.

What values for α are possible? Why?

$\alpha = \pm 1, 0$. **Otherwise, a sinusoidal input at frequency ω would not elicit a sinusoidal output at the same frequency. To get frequency in the output different than the drive, the circuit must be nonlinear and you can't build a nonlinear circuit with ideal resistors, inductors and capacitors.**